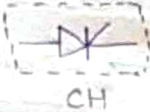
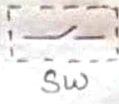


## UNIT - III

### CONTROL OF DC MOTORS BY CHOPPERS

Chopper: Chopper is a static semiconductor device which converts fixed DC into variable DC directly.

It is represented by  (Or) 

Chopper acts as switch i.e., it connects supply to load or disconnects supply to load.

Advantages of choppers:

1. Fast response
2. Smooth control
3. High efficiency
4. Regeneration.

Applications of choppers:

1. Battery operated vehicles
2. Trolley buses
3. Subway cars
4. Traction-motor control.


Classification of choppers: [Types]

Choppers are classified into two types. They are:

1. AC choppers
2. DC choppers

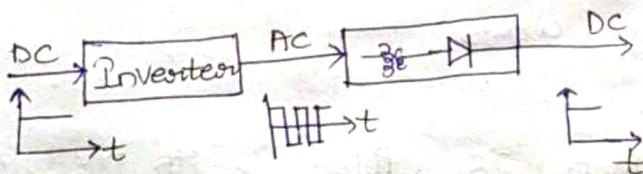
1. AC choppers:

In case of AC link chopper, first DC is converted to AC with help of inverter. After that AC is stepped up or stepped down by a transformer, which is then converted back to DC by a rectifier.



AC link chopper is costly, bulky and less efficient as conversion done in two stages.

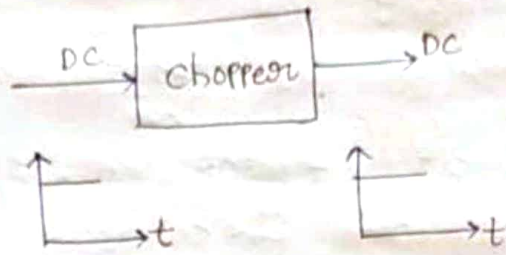2. DC chopper: It is a static device that converts fixed dc input voltage to variable dc output voltage directly.



This kind of choppers are more efficient as they involve only one stage conversion.

Control strategies of choppers:

In case of AC, current control otherwise known as firing angle control is involved.

In case of DC, voltage control is involved.

The variable dc voltage is controlled by varying ON and OFF times of converter.

Frequency of operation is given by

$$f_c = \frac{1}{t_{ON} + t_{OFF}} = \frac{1}{T}$$

Duty cycle/ratio is given by  $\delta = \frac{t_{ON}}{t_{ON} + t_{OFF}} = \frac{t_{ON}}{T}$

Duty cycle varies from 0 to 1 and it should not vary beyond 1.

There are two control strategies in choppers:


1. Time ratio control strategy (TRC)
2. Current limit control strategy (CLC)

1. Time ratio control strategy: It can be achieved in two ways

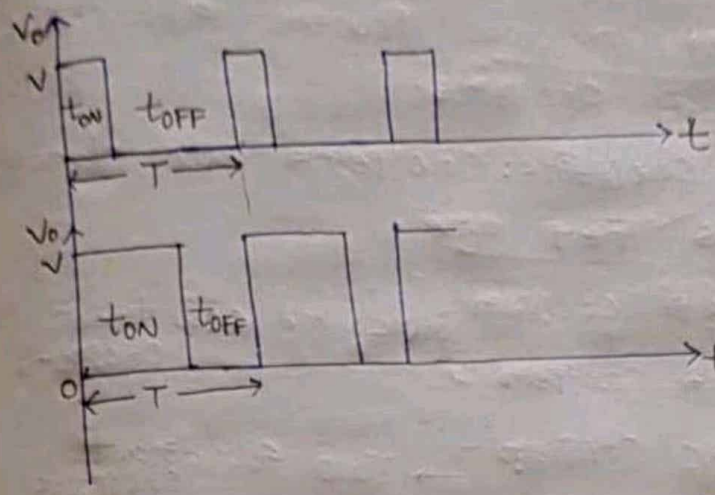(i) Constant frequency:


It is also known as pulse width modulation and is used in inverters.

In this method, either ON time or OFF time can be varied but total time period is constant.



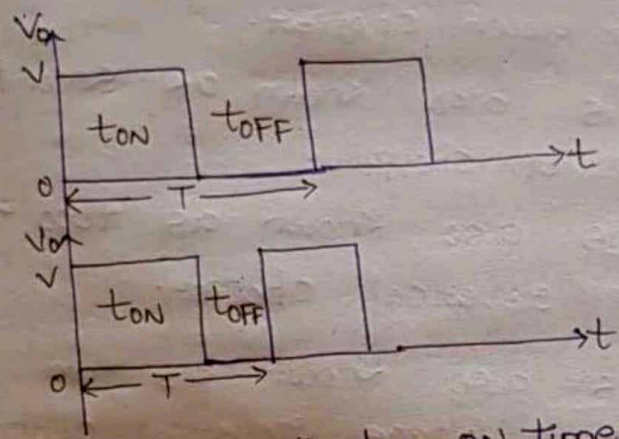b) Variable Frequency:


It is also known as frequency modulation and is applicable in radio signals in electronics.



In this method, ON time, OFF time and total time period can be varied such that frequency is varied ( $\because f = \frac{1}{T}$ )

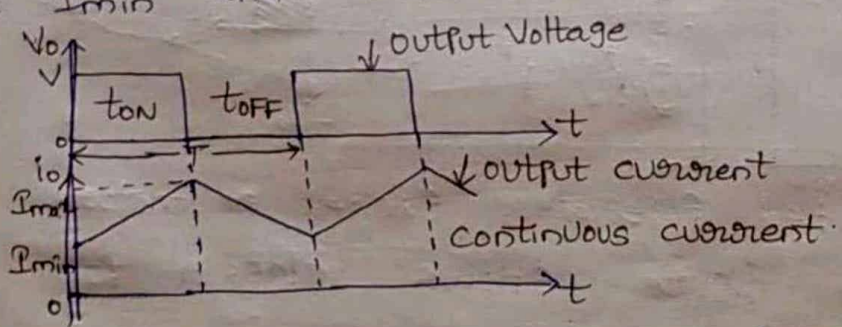2. Current Limit Control Strategy:

In this method, current is maintained in between minimum and maximum limits i.e  $I_{min}$  and  $I_{max}$  as shown in figure below



When current is minimum, device is in ON state and when current is maximum

device is in off state.

$t_{on} > t_{off}$  ( $\alpha < 90$ )  $\rightarrow$  continuous mode

$t_{on} < t_{off}$  ( $\alpha > 90$ )  $\rightarrow$  discontinuous mode.

It is preferred in low power applications and is used in choppers.

Classification of choppers: Choppers are classified into five types. They are

1. Type A (or) class A chopper  $\rightarrow$  single quadrant choppers
2. Type B (or) class B chopper  $\rightarrow$  single quadrant choppers
3. Type C (or) class C chopper  $\rightarrow$  two quadrant choppers
4. Type D (or) class D chopper  $\rightarrow$  two quadrant choppers
5. Type E (or) class E chopper  $\rightarrow$  four quadrant choppers

Type A chopper is also known as first quadrant or step down chopper.

Type B chopper is also known as second quadrant or step up chopper.

Type C chopper is also known as two quadrant type A or current reversal chopper.

Type D chopper is also known as two quadrant type B or voltage reversal chopper.

1. Type A (or) class A (or) step down chopper (or) motoring chopper (or) Buck Converter: Fed separately excited DC motor:

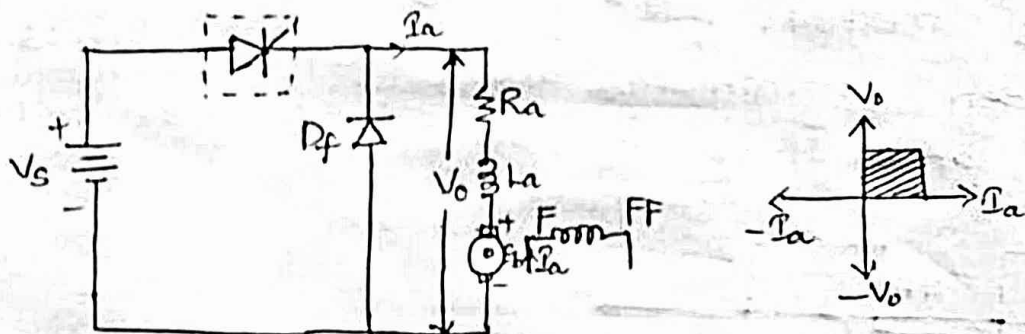


Fig. Class A <sup>chopper</sup> Fed Separately Excited DC motor.

The above figure shows class A fed separately excited DC motor.

When  $CH_1$  is in ON state, current starts flowing through  $V_s - CH_1 - R_a - L_a - E_b - V_s$  and voltage will appear across load.

$$V_o = V_s$$

It is known as duty interval.

$$V_o = I_a R_a + L_a \frac{dI_a}{dt} + E_b = V_s \quad ; \quad 0 < t < T_{ON}$$

When  $CH_1$  is in OFF state, current starts flowing through  $R_a - L_a - E_b$  and it forms a closed path.

$$\text{Hence } V_o = 0$$

It is known as freewheeling interval.

$$\therefore V_o = 0 = I_a R_a + L_a \frac{dI_a}{dt} + E_b \quad ; \quad T_{ON} < t < T$$

It was observed that,

When  $CH_1$  is in ON state,  $V_o = V_s$ .

$CH_1$  is in OFF state,  $V_o = 0$ .

$$\text{Output Voltage, } V_o = \frac{1}{T} \int_0^{T_{ON}} V_s \cdot dt + \int_{T_{ON}}^T V_o \cdot dt$$

$$= \frac{V_s}{T} (T_{ON} - 0) + 0$$

$$V_o = \frac{V_s}{T} \cdot T_{ON}$$

$$V_o = \delta V_s \quad \text{where } \delta = \frac{T_{ON}}{T}$$

' $\delta$ ' varies from 0 to 1.

It was observed that power is delivered from source to load. Hence it is known as motoring chopper. (or) step down chopper. Since  $V_o < V_s$ .

Both voltage and current are positive. Hence class A chopper is also known as first quadrant chopper.

Output waveforms:

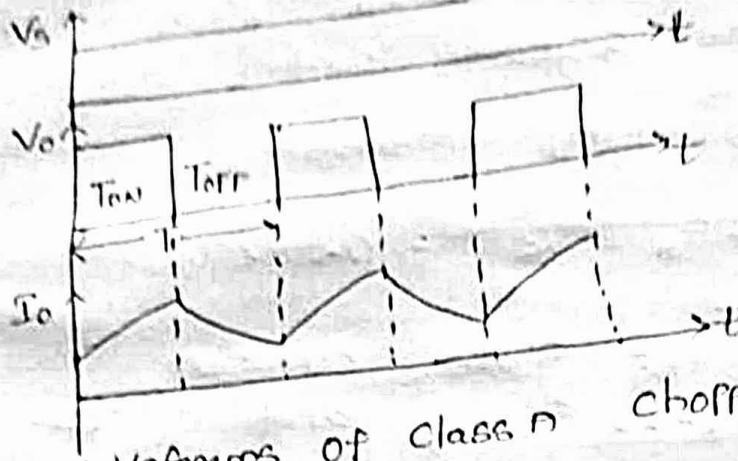


Fig. waveforms of class A chopper fed dc separately excited DC motor:

Speed-Torque characteristics:

We know that,

For separately excited DC motor,

$$E_b = V_o - I_a R_a$$

$$V_o = E_b + I_a R_a$$

$$\text{But } E_b = K_m \cdot \omega_m$$

$$\text{Torque } T = K_a \phi I_a$$

$$\Rightarrow I_a = \frac{T}{K_a \phi}$$

$$V_o = \delta V_s$$

$$K_m \omega_m = \delta V_s - \frac{T}{K_a \phi} \cdot R_a$$

$$\Rightarrow \omega_m = \frac{\delta V_s}{K_m} - \frac{T}{(K_a \phi)^2} \cdot R_a$$

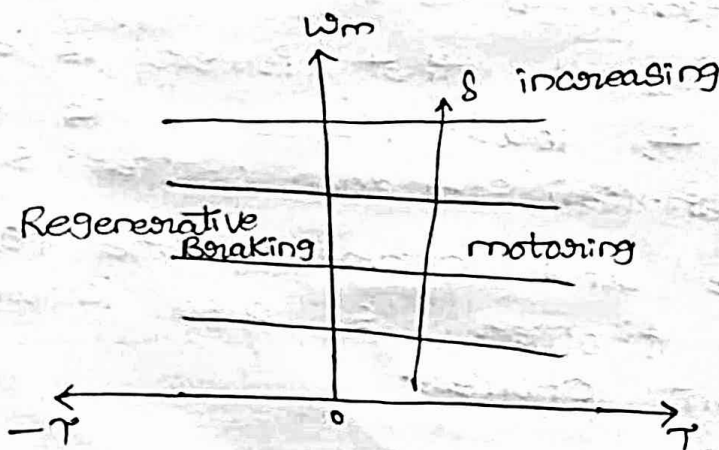


Fig. Torque Speed characteristics of class A chopper fed separately excited DC motor.

class A chopper: fed DC series motor:


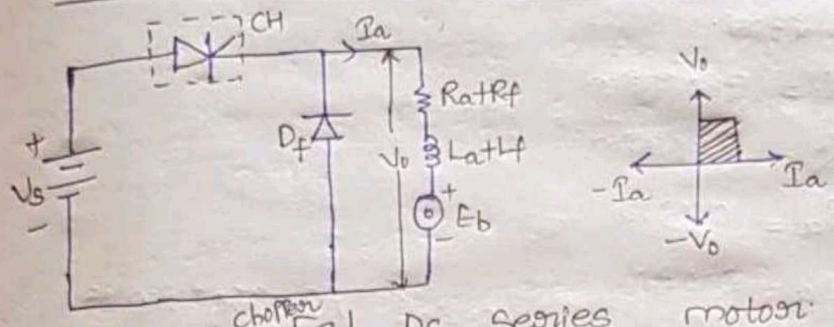
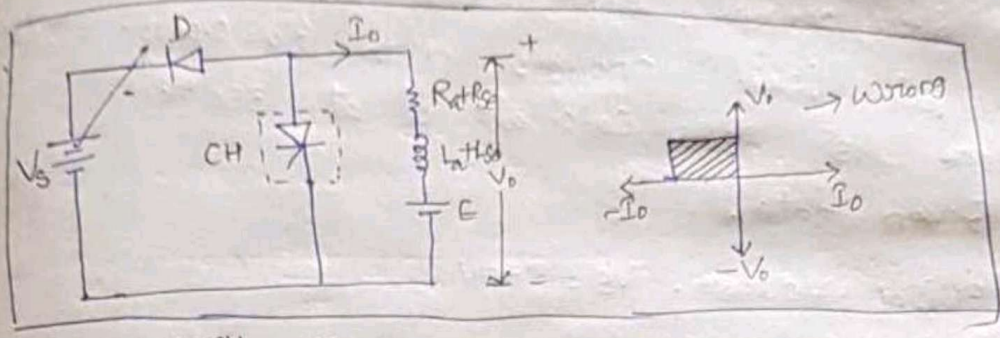


Fig. class A <sup>chopper</sup> Fed DC series motor

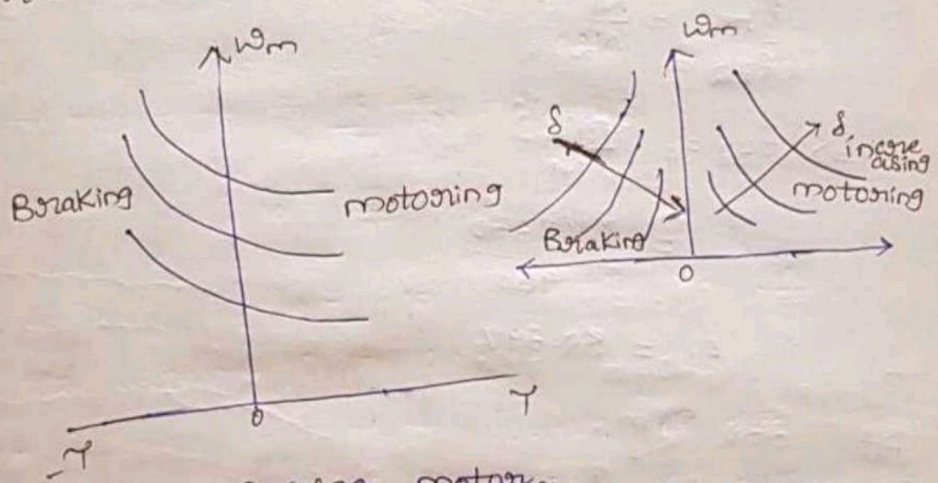All explanation and output voltage expression, waveforms are as same as separately excited DC motor. But only change in speed torque characteristics as follows:  
 Speed-Torque characteristics:



w.k.t, For DC series motor,

$$E_b = V_0 - I_a(R_a + R_f)$$

$$E_b = K_{af} \cdot I_a \cdot N + K_{res} \cdot N$$

$$T = K_{af} \cdot I_a^2 \quad ; \quad N = \frac{V_0 - I_a(R_a + R_f)}{K_{af} \cdot I_a + K_{res}}$$

$$I_a = \sqrt{\frac{T}{K_{af}}}$$

$$\Rightarrow K_{af} \cdot I_a N + K_{res} \cdot N = 8V_0 - \sqrt{\frac{T}{K_{af}}} \cdot (R_a + R_f)$$

Problems:  
 1. A 230V, 960rpm, 200A separately excited dc motor  
 is fed from chopper with  $R_a = 0.02\Omega$ . Supply  
 voltage is 230V. Calculate 's' at 350 rpm.  
 Sol Given data,

Supply voltage,  $V_s = 230V$

Speed  $V_o = 230V$   
 $N_1 = 960 \text{ rpm}$   
 $N_2 = 350 \text{ rpm}$   
 $R_a = 0.02\Omega$   
 $I_a = 200A$

Back emf at rated speed  $N = 960 \text{ rpm}$  is

$$E_{b1} = V_o - I_a R_a$$

$$= 230 - 200 \times 0.02$$

$$E_{b1} = 226V$$

We know that,

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\Rightarrow E_{b2} = \frac{E_{b1} \cdot N_2}{N_1}$$

$$= \frac{226 \times 350}{960}$$

$$E_{b2} = 82.39V$$

At 350 rpm,

$$E_{b2} = V_o - I_a R_a$$

$$\Rightarrow E_{b2} = V_o - I_a R_a$$

$$V_o = E_{b2} + I_a R_a$$

$$= 82.39 + 200 \times 0.02$$

$$V_o = 86.39V$$

where  $V_o = s \cdot V_s$

$$s = \frac{V_o}{V_s} = \frac{86.39}{230} = 0.37$$



2. A 230V, 24A, 1000rpm Separately excited dc motor with  $R_a = 2\Omega$  is controlled by chopper at 500Hz,  $V_{ac} = 230V$ . Calculate duty ratio for 1/2 times rated motor torque at 500rpm

Sol Given data,

$$V_0 = 230V$$

$$I_a = 24A$$

$$N_1 = 1000\text{rpm}$$

$$R_a = 2\Omega$$

$$F = 500\text{Hz}$$

$$V_{ac} = 230V$$

We know that,

$$F = \frac{1}{T} = \frac{1}{500} = 0.002 = 2 \times 10^{-3} \text{ sec}$$

$$E_{b1} = V_0 - I_a R_a \\ = 230 - (24 \times 2)$$

$$E_{b1} = 182V$$

We know that,

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\Rightarrow E_{b2} = \frac{E_{b1} \cdot N_2}{N_1} = \frac{182 \times 500}{1000} = 91V$$

$$E_{b2} = V_0 - I_a R_a$$

$$V_0 = E_{b2} + I_a R_a = 91 + 1.2 \times 24 \times 2$$

$$V_0 = 139V \quad 148.6V$$

$$\delta = \frac{V_0}{V_s} = \frac{148.6}{230} = 0.646$$

3. A chopper is used to ON or OFF separately excited dc motor with  $V_s = 230V$ ,  $T_{on} = 10ms$ ,

$T_{off} = 15ms$ . Calculate average load current when motor speed is 1500rpm and  $K_m = 0.5 \text{ Vs/rad}$

Sol Given data,

$$V_s = 230V$$

$$T_{on} = 10ms$$

$$T_{off} = 15 \text{ ms}$$

$$\text{Speed} = 1500 \text{ rpm}$$

$$K_m = 0.5 \frac{\text{V} \cdot \text{sec}}{\text{rad}}$$

we know that,

$$E_b = K_m \cdot \omega_m$$

$$= 1500 \times 0.5 \times \frac{2\pi N}{60}$$

$$E_b = 0.5 \times \frac{2\pi \times 1500}{60} = 78.539 \text{ V}$$

$$\delta = \frac{T_{on}}{T} = \frac{10}{10+15} = \frac{10}{25}$$

$$\delta = 0.4$$

$$V_o = \delta \cdot V_s = 230 \times 0.4 = 92 \text{ V}$$

$$E_b = V_o - I_a R_a$$

$$\text{Assume } R_a = 1$$

$$E_b = V_o - I_a$$

$$78.53 = 92 - I_a$$

$$-I_a = 78.53 - 92$$

$$-I_a = -13.47 \text{ A}$$

$$I_a = 13.47 \text{ A}$$

Type-B Chopper Fed Separately Excited DC motor:

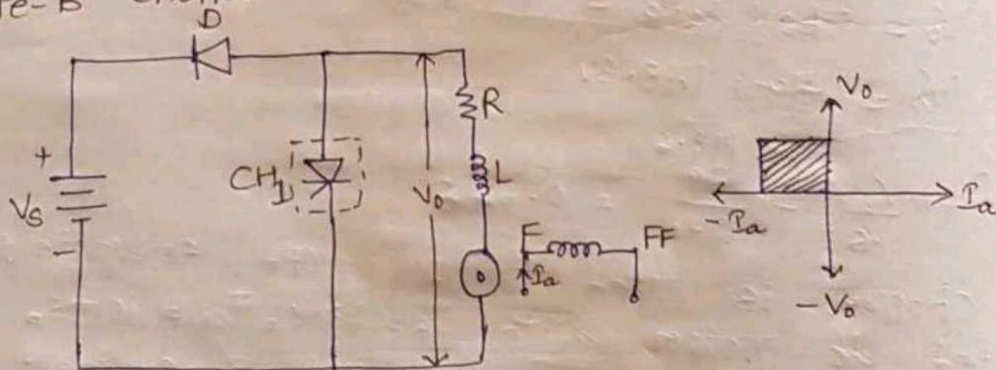


Fig. Class B ↑ Fed Separately excited DC motor.

The above figure shows the class B Chopper fed separately excited DC motor.

when  $CH_1$  is in ON state,  $E_b$  will act as source. Current flows through  $E_b+ - L_a - R_a - CH_1 - E_b-$  and it forms a closed path. Hence  $V_o = 0$ .

Energy is stored in inductor. This interval is known as energy storage interval.

Hence  $V_o = 0$

$$V_o = I_a R_a + L_a \frac{dI_a}{dt} + E_b = 0 ; 0 < t < T_{ON}$$

when  $CH_1$  is in OFF state,  $D_f$  is in forward bias and energy is dissipated from inductor through  $E_b - L_a - R_a - D_f - V_s+ - V_s-$

Hence  $V_o = V_s$ .

It is known as duty interval.

$$V_o = I_a R_a + L_a \frac{dI_a}{dt} + E_b = V_s ; T_{ON} < t < T_{OFF}$$

It was observed that,


when  $CH_1$  is in ON state,  $V_o = 0$

$CH_1$  is in OFF state,  $V_o = V_s$ .

Class B chopper is also known as step-up chopper (or) Boost converter. Since  $V_o > V_s$

It was observed that power is delivered from load to source. Hence class B chopper is also known as Regenerative Braking chopper.

Output waveforms:

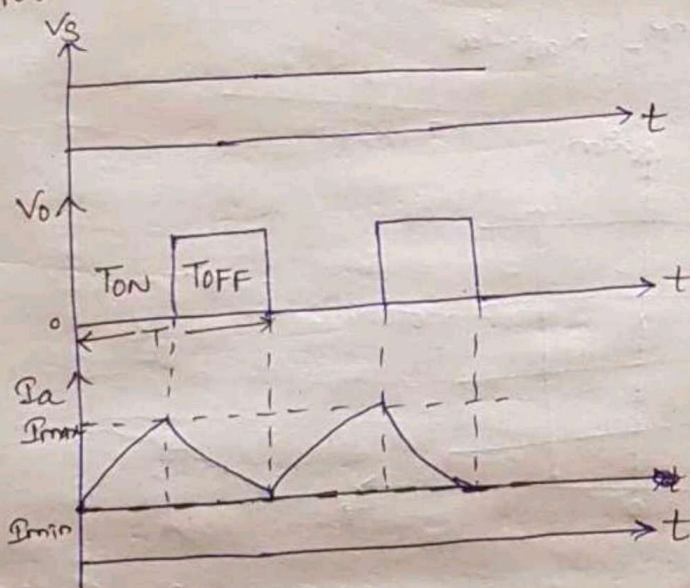

Average output Voltage,

$$V_o = \frac{1}{T} \left[ \int_{T_{ON}}^T V_s \cdot dt + \int_0^{T_{ON}} V_s \cdot dt \right]$$

$$\therefore V_0 = \frac{V_s}{T} [T - T_{0N}]$$

$$= V_s \left[ \frac{T - T_{0N}}{T} \right]$$

$$= V_s \left[ 1 - \frac{T_{0N}}{T} \right]$$

$$V_s = V_0 (1 - s)$$

$$V_0 = \frac{V_s}{1 - s}$$

$$V_0 > V_s$$

where 's' varies from '0' to '1'

Speed-Torque characteristics:

At starting, only motoring action takes place

$$\therefore E_b = V_0 + I_a R_a$$

But due to regenerative braking, back emf becomes:

$$E_b = V_0 + I_a R_a$$

$$\text{where } V_0 = \frac{V_s}{1 - s}$$

$$E_b = K_m \omega_m$$

$$N = \frac{V_0 + I_a R_a}{K_m}$$

$$T = K_a \phi I_a$$


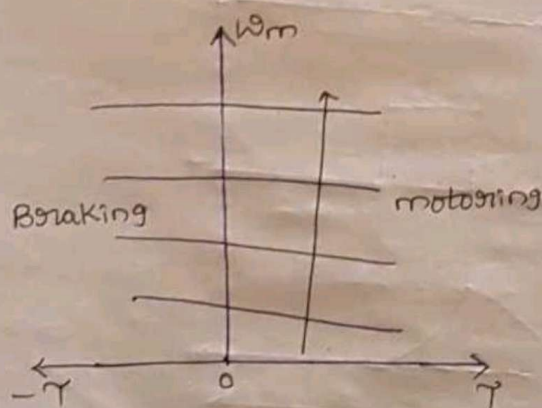
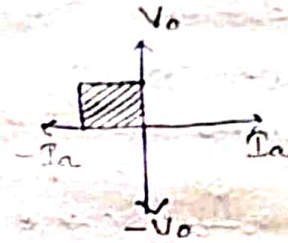



Fig. Torque speed characteristics of class B fed separately excited DC motor.

# TYPE B Chopper Fed Dc Series motor:

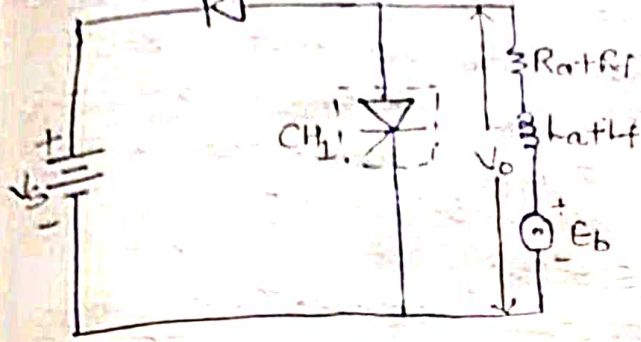

Explanation, output = Voltage expressions and waveforms are same as Type B chopper fed separately excited DC motor.

Speed - Torque characteristics:

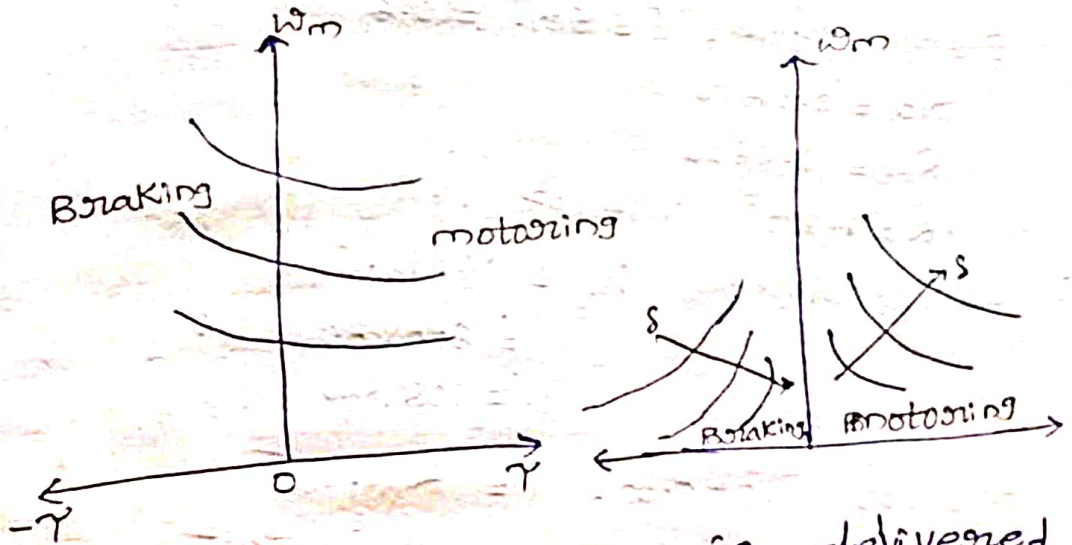

In Type B, chopper power is delivered from load to source. Hence it is also known as regenerative braking chopper.

$$\therefore E_b = V_o + I_a(R_a + R_f)$$

$$E_b = K_a \cdot I_a \cdot N + K_{res} \cdot N$$

$$T = K_a \cdot I_a^2$$

where  $V_o = \frac{V_s}{1-s}$

$$N = \frac{V_o - I_a(R_a + R_f)}{K_a \cdot I_a + K_{res}}$$

Problems:

A DC series motor is fed from 600V DC source through a chopper. The DC motor has the following parameters: The average armature current of 300A is ripple free. From a chopper duty cycle of 60%, determine

- (i) Input Power from source.  
(ii) motor speed and motor torque.

$$R_a = 0.04 \Omega, R_s = 0.06 \Omega, K = 4 \times 10^{-3} \text{ Nm/Amp}^2$$

Sol) Given data,

$$V_s = 600 \text{ V}$$

$$I_a = 300 \text{ A}$$

$$\text{Duty cycle, } \delta = 60\% = 0.6$$

$$R_a = 0.04 \Omega$$

$$R_s = 0.06 \Omega$$

$$K = 4 \times 10^{-3} \text{ Nm/Amp}^2$$

$$\begin{aligned} \text{(i) Input Power } P_{in} &= V_s \cdot I_a \cdot \delta \\ &= 600 \times 300 \times 0.6 \\ P_{in} &= 108 \text{ Kw} \end{aligned}$$

$$\begin{aligned} \text{(ii) motor Torque, } T &= K_m \cdot I_a^2 \\ &= 4 \times 10^{-3} \times 300^2 \\ &= 360 \text{ N-m} \end{aligned}$$

$$N = \frac{V_o - I_a(R_a + R_s)}{K_a \cdot I_a}$$

$$V_o = \delta V_s$$

$$= 0.6 \times 600$$

$$V_o = 360 \text{ V}$$

$$N = \frac{360 - 300(0.04 + 0.06)}{4 \times 10^{-3} \times 300}$$

$$N = 275 \text{ rad/sec}$$

$$= 28.79 \text{ rpm}$$

Class C chopper (Two-quadrant Type-A chopper) fed separately excited DC motor:

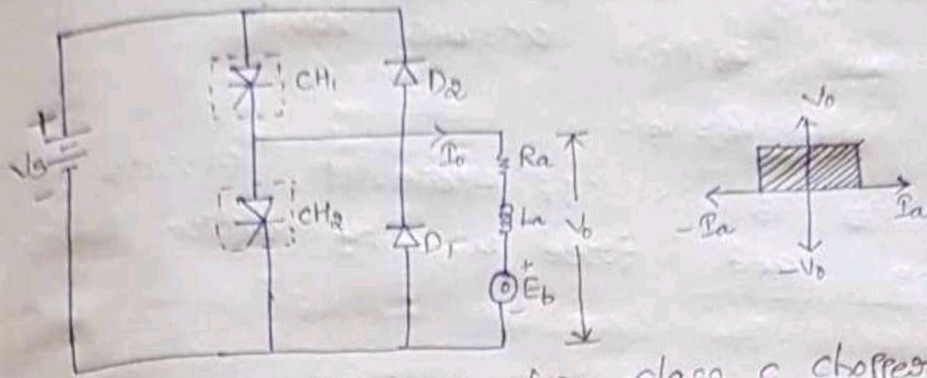


Fig. circuit Diagram for class C chopper fed separately excited DC motor.

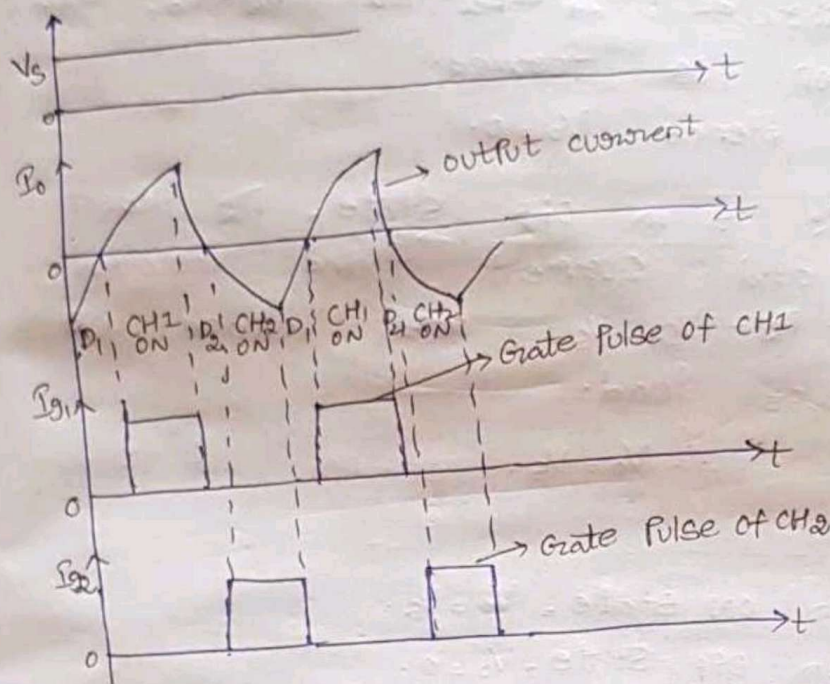


Fig. waveforms.

Above figure shows circuit diagram and waveforms of class C chopper fed separately excited DC motor.

It is a two quadrant chopper also known as two quadrant Type A chopper.

It is the combination of class A and class B choppers.

$CH_1$  and  $D_1$  constitutes the class A chopper.

$CH_2$  and  $D_2$  constitutes class B chopper.

when  $CH_1$  is in ON state, current starts flowing through  $V_s - CH_1 - R_a - L_a - E_b$ .  
Voltage will appear across load.  
 $\therefore V_o = V_s$ .

when  $CH_1$  is in OFF state,  $D_1$  starts conducting and free wheeling action takes place.  
Hence  $V_o = 0$ .

when  $CH_2$  is in ON state, current starts flowing through  $E_b - L_a - R_a - CH_2 - E_b$  and closed loop is formed.  
Hence  $V_o = 0$ .

when  $CH_2$  is in OFF state,  $D_2$  starts conducting and current flows through  $E_b - L_a - R_a - D_2 - V_s - V_s$  and voltage will appear across load.  
 $\therefore V_o = V_s$ .

When,

$CH_1$  is in ON state,  $V_o = V_s$ .

$CH_1$  is in OFF state,  $V_o = 0$ .

$CH_2$  is in ON state,  $V_o = 0$ .

$CH_2$  is in OFF state,  $V_o = V_s$ .

It was observed that voltage remains same and current becomes reversed.

Hence class C chopper is also known as current reversal chopper.



Torque - speed characteristics:

W.K.T,

For Separately excited DC motor

$$E_b = V_o - I_a R_a$$

$$V_o = E_b + I_a R_a$$

$$T = K_a \phi \cdot I_a$$

$$N = \frac{V_o - I_a R_a}{K_a \phi}$$

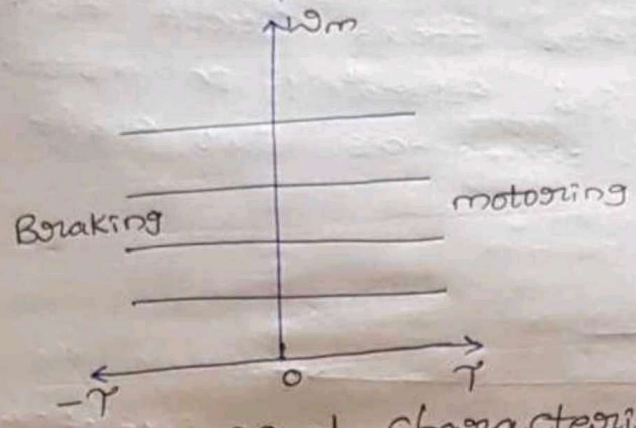


Fig. Torque speed characteristics for class c fed separately excited DC motor.

For DC Series motor,

$$E_b = V_o - I_a (R_a + R_f)$$

$$E_b = K_a \phi \cdot I_a \cdot N + K_{res} \cdot N$$

$$T = K_a \phi \cdot I_a^2$$

$$N = \frac{V_o - I_a (R_a + R_f)}{K_a \phi + K_{res}}$$

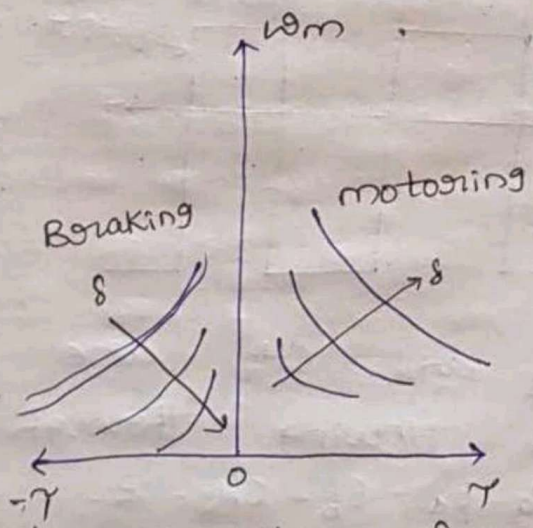


Fig. N-T characteristics for class c fed DC Series motor.

# Class D <sup>chopper</sup> Fed Separately Excited DC motor:


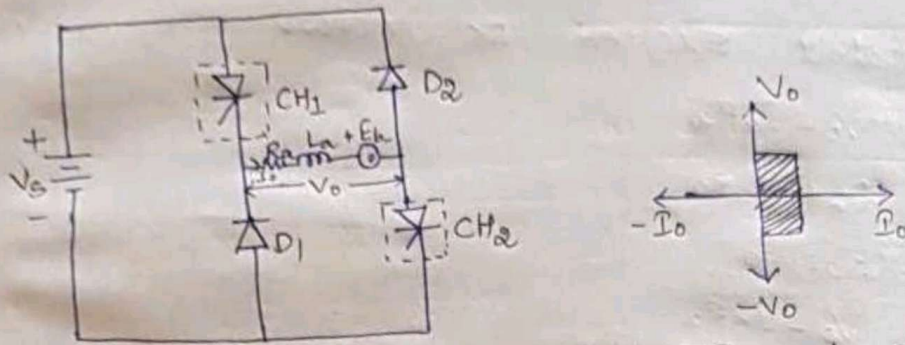


Fig. class D Fed Separately Excited DC motor  
 The above figure shows circuit diagram from class D Fed Separately DC motor.  
 It is also known as two quadrant

type-B chopper waveforms:

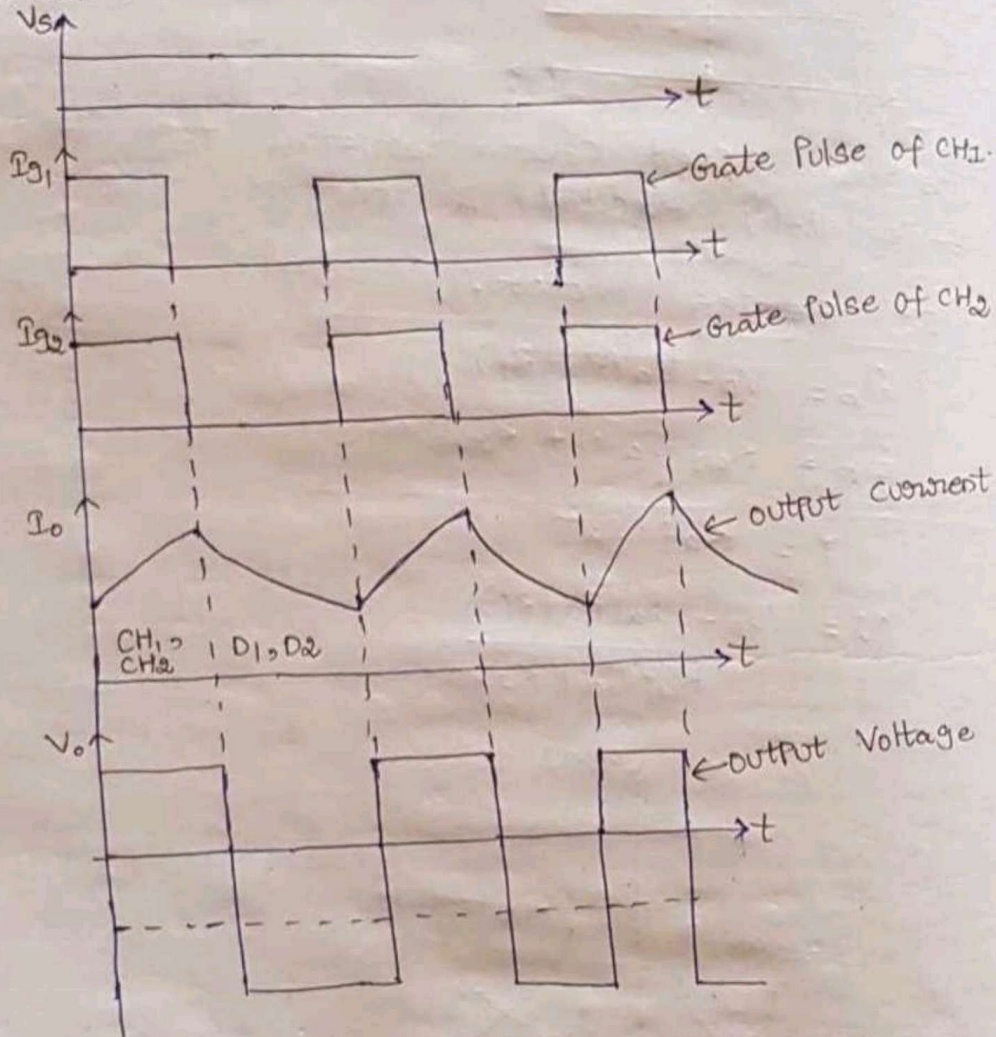

when both  $CH_1$  and  $CH_2$  are in on state current starts flowing through the path  $V_s \rightarrow CH_1 \rightarrow R_a \rightarrow L_a \rightarrow E_b \rightarrow CH_2 \rightarrow V_s$  and voltage will appear across load.  
 $\therefore V_o = V_s$

When both  $CH_1$  and  $CH_2$  are in off state current starts flowing through the path  $E_b - R_a - V_s - V_s - D_1 - R_a - I_a$  and negative voltage will appear across load.  
Hence  $V_o = -V_s$ .

It was observed that reversal of voltage takes place.

Hence type D chopper is also known as voltage reversal chopper.


Speed-Torque characteristics:

For separately excited DC motor,

$$E_b = V_o - I_a R_a$$

$$\tau = K_a \phi I_a$$

$$N = \frac{V_o - I_a R_a}{K_a \phi}$$

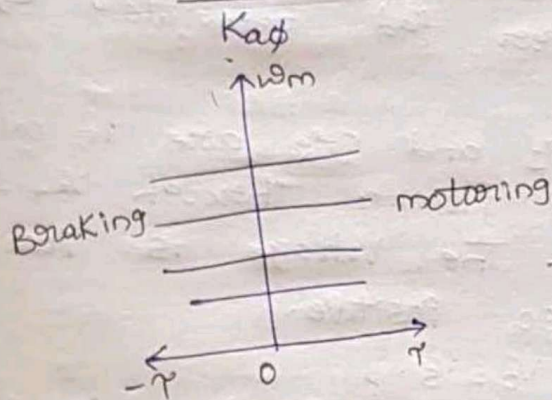


For DC series motor,

$$E_b = V_o - I_a (R_a + R_f) = K_a \phi I_a N + K_{res} \cdot N$$

$$\phi = K_a \phi I_a^2$$
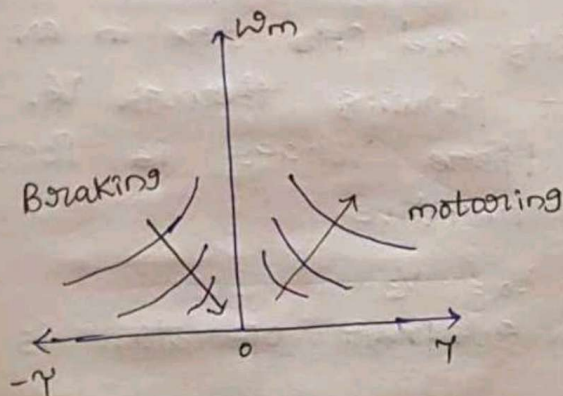
$$N = \frac{V_o - I_a (R_a + R_f)}{K_a \phi I_a + K_{res}}$$



# Type E chopper Fed Separately Excited DC motor


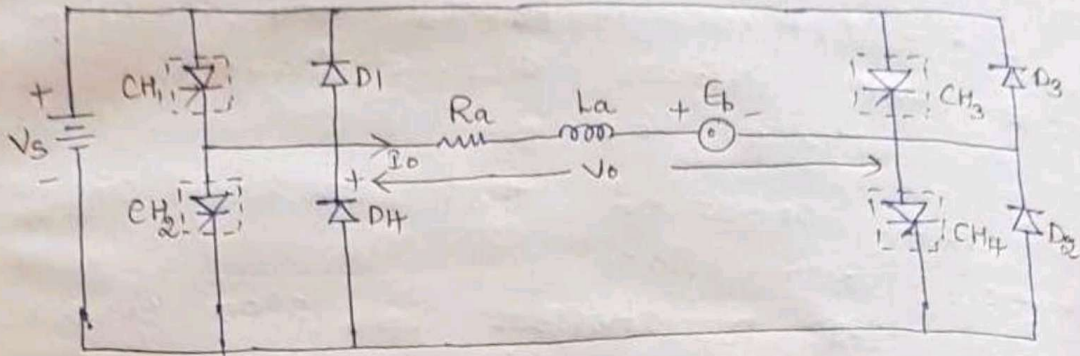


Fig. Type E chopper fed separately excited DC motor

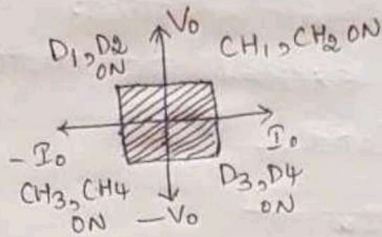

The above figure shows circuit diagram of class E chopper fed separately excited DC motor.

When both  $CH_1$  and  $CH_2$  are in ON state current starts flowing through  $V_s^+ - CH_1 - R_a - L_a - E_b - CH_2 - V_s^-$ . The voltage is positive and current is also positive.

$$\therefore V_o = V_s$$

Hence first quadrant operation is obtained.

When both  $CH_1$  and  $CH_2$  are in OFF state then current starts flowing through

$$E_b - D_3 - V_s^+ - V_s^- - D_4 - R_a - L_a$$

$\therefore$  Voltage is negative and current is positive

$$V_o = -V_s$$

Hence fourth quadrant operation is obtained.

When both  $CH_3$  and  $CH_4$  are in ON state,

current starts flowing through  $V_s^+ - CH_3 - E_b - L_a - R_a - CH_4 - V_s^-$ . Here voltage is positive and current is negative

$$\therefore V_o = -V_s$$

Hence third quadrant operation is obtained.


when both  $C1_3$  and  $C1_4$  are in off state,  
current start flowing through  $E_b - L_a - R_a - D_1 -$   
but  $V_b = V_a$ . current direction is reversed  
voltage is positive  
 $\therefore V_o = V_a$

Hence second quadrant operation is obtained.

It was observed that four quadrant  
operation is obtained by using class E  
chopper.

Hence it is also known as four  
quadrant chopper.

## Dynamic Braking of choppers:

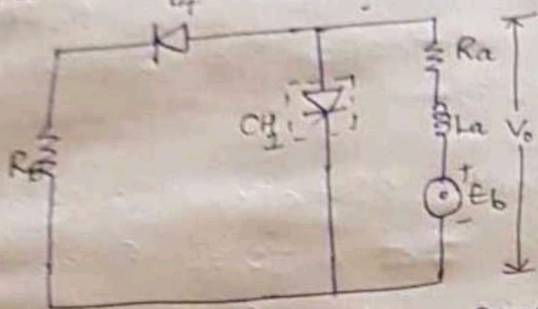

when armature resistance is disconnected from source and is connected across a resistance then it is known as dynamic braking.

Dynamic braking is also known as rheostatic braking.

Here motor armature is disconnected from source and braking resistance is connected in series with armature.

when  $CH_1$  is in ON state armature is short circuited and resistance across terminals is zero.

when  $CH_1$  is in OFF state, the resistance across terminals is  $R_B$ .

$$R = R_B \left[ \frac{T}{T} - \frac{T_{ON}}{T} \right]$$

$$= R_B \left[ \frac{T - T_{ON}}{T} \right]$$

$$R_{eff} = R_B [1 - \delta] \quad ; \quad \delta \text{ varies from '0' to '1'}$$


Above equation shows that the effective value of braking resistor can be changed steplessly from 0 to  $R_B$  as  $\delta$  is controlled from 0 to 1.

$$\text{i.e. } R = R_B \text{ when } \delta = 0$$

$$R = 0 \text{ when } \delta = 1.$$

Back emf expression is given by

$$E_b = I_a [R_a + R_B(1 - \delta)]$$

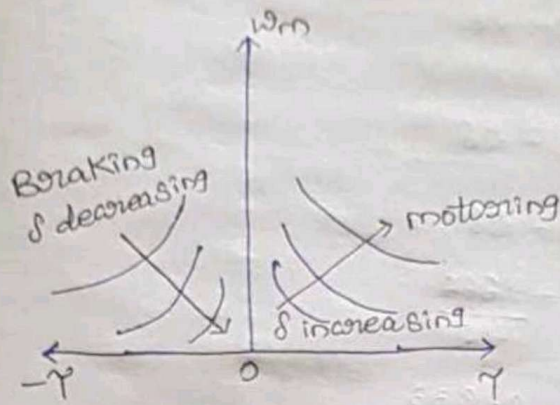

problems:

1. A 230V, 960 rpm, 200A separately excited DC motor has  $R_a = 0.02 \Omega$ . motor is operated in dynamic braking with braking resistance of  $2 \Omega$ .
- (i) calculate duty cycle ratio for motor speed of 600 rpm when braking torque is equal to twice the rated torque.
- (ii) what will be motor speed of duty cycle 0.6 when braking torque is equal to twice the rated torque.

Sol Given data,

$$V_0 = 230V$$

$$N_1 = 960 \text{ rpm}$$

$$I_a = 200A$$

$$R_a = 0.02 \Omega$$

$$R_B = 2 \Omega$$

(i)  $N_2 = 600 \text{ rpm}$

$$I_a = 2I_a$$

$$E_{b1} = V_0 - I_a R_a$$

$$= 230 - 200 \times 0.02$$

$$= \cancel{226} + 226 \text{ V}$$

W.K.T,

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$E_{b2} = \frac{E_{b1} \cdot N_2}{N_1} = \frac{226 \times 600}{960} = 141.25 \text{ V}$$

$$E_{b2} = I_a [R_a + R_B(1-\delta)]$$

$$\Rightarrow 141.25 = 400 [0.02 + 2(1-\delta)]$$

$$\frac{141.25}{400} = 0.02 + 2 - 2s$$

$$\frac{141.25}{400} - 2.02 = -2s$$

$$-1.666 = -2s$$

$$s = \frac{-1.666}{-2}$$

$$s = 0.833$$

$$\begin{aligned} \text{(ii) } E_{b2} &= I_a [R_a + R_B(1-s)] \\ &= 400 [0.02 + 2(1-0.6)] \\ &= 328V \end{aligned}$$

W.K.T,

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2} \Rightarrow N_2 = \frac{N_1 \cdot E_{b2}}{E_{b1}}$$

$$= \frac{960 \times 328}{226}$$

$$N_2 = 1393 \text{ rpm}$$

Closed loop operation of DC motor using chopper:

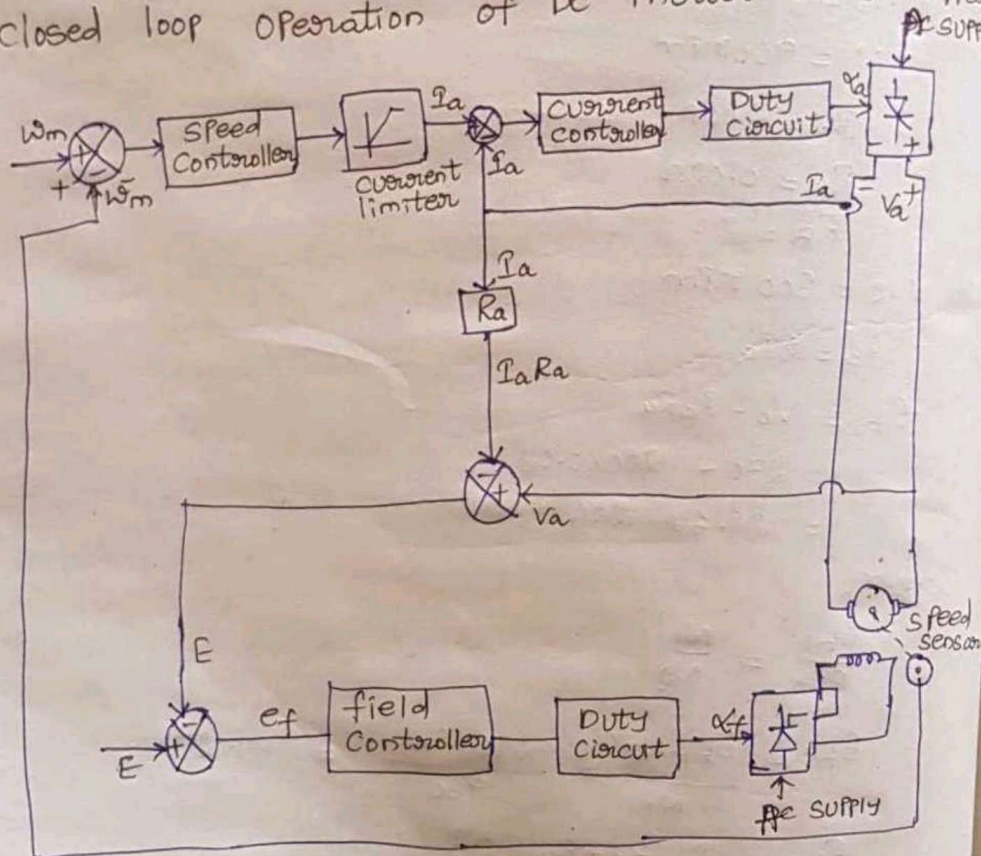


Fig. closed loop control scheme for control below and above base speed.



The closed loop operation of DC motor using choppers is shown in figure.

It consists of two loops namely

1. Inner current control loop
2. Outer speed control loop.

The main purpose of closed loop operation is:

1. Protection
2. Enhancement of speed
3. Steady state accuracy.

Whenever there is increase in reference speed  $\omega_m$ , it produces positive speed error and it is passed through speed controller and output of speed controller is applied to current limiter, it saturates for even small speed error. It sets the value of current of maximum allowable value in order to vary duty cycle/ratio. It should be in the range of 0 to 1.

If it is not set, by default more current will apply to duty circuit and there is a chance of damage.

This method of action is known as motoring.

When reference speed  $\omega_m$  is decreased which produces negative speed error, it is passed through speed controller, then it is passed to current limiter, it saturates for even small speed error. It was passed through current controller and it will set maximum allowable current for duty circuit in order to run circuit in safer mode.

' $\delta$ ' should be in range of 0 to 1. This method of action is known as braking.

In this manner both motoring and braking actions were achieved by using closed loop operation of choppers.

The type of controllers used were P, PI and PID controllers.