

Summary

Serial No.	Type of converter	Load	Parameter
1.	1 ϕ half wave	R RL RL with freewheeling diode	$V_{o(av)} = \frac{V_m}{2\pi} (1 + \cos \alpha)$ $V_{o(av)} = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$ $V_{o(av)} = \frac{V_m}{2\pi} (1 + \cos \alpha)$

2.	1 ϕ semi converter	<p>R</p> <p>RL</p> <p>RL</p>	$V_{o(av)} = \frac{V_m}{\pi} (1 + \cos \alpha)$ $V_{o(rms)} = \left\{ \frac{V_m^2}{2\pi} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right] \right\}^{\frac{1}{2}}$ $V_{o(av)} = \frac{V_m}{\pi} (1 + \cos \alpha)$ $V_{o(rms)} = \left\{ \frac{V_m^2}{2\pi} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right] \right\}^{\frac{1}{2}}$ $DF = \cos \frac{\alpha}{2}$ $PF = \sqrt{\frac{8}{\pi(\pi - \alpha)}} \cos^2 \frac{\alpha}{2}$ $HF = \frac{\sqrt{\pi(\pi - \alpha)} - 1}{\sqrt{8 \cos^2 \frac{\alpha}{2}}}$
3.	1 ϕ full converter	<p>R</p> <p>RL</p> <p>RL with freewheeling diode</p> <p>RL</p>	$V_{o(av)} = \frac{V_m}{\pi} (1 + \cos \alpha)$ $V_{o(rms)} = \left\{ \frac{V_m^2}{2\pi} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right] \right\}^{\frac{1}{2}}$ $V_{o(av)} = \frac{2V_m}{\pi} \cos \alpha$ $V_{o(rms)} = \frac{V_m}{\sqrt{2}}$ $V_{o(av)} = \frac{V_m}{\pi} (1 + \cos \alpha)$ $V_{o(rms)} = \left\{ \frac{V_m^2}{2\pi} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right] \right\}^{\frac{1}{2}}$ $DF = \cos \alpha$ $PF = \frac{2\sqrt{2}}{\pi} \cos \alpha$ $HF = 0.4834 \text{ or } 48.34\%$
4.	3 ϕ halfwave converter	<p>R</p> <p>RL</p>	$V_{o(av)} = \frac{3\sqrt{3} V_m}{2\pi} \cos \alpha \text{ for } \alpha \leq 30^\circ$ $= \frac{3V_m}{2\pi} \left[1 + \cos \left(\frac{\pi}{6} + \alpha \right) \right] \text{ for } \alpha > 30^\circ$ $V_{o(av)} = \frac{3\sqrt{3} V_m}{2\pi} \cos \alpha$

5.	3 ϕ semiconverter	R, RL	$V_{o(av)} = \frac{3\sqrt{3}V_m}{2\pi} (1 + \cos \alpha)$ ✓
6.	3 ϕ fullconverter	R RL RL - with freewheeling diode	$V_{o(av)} = \frac{3\sqrt{3}V_m}{\pi} \cos \alpha$ for $\alpha \leq 60^\circ$ $V_{o(av)} = \frac{3\sqrt{3}V_m}{\pi} \left[1 + \cos \left(\frac{\pi}{3} + \alpha \right) \right]$ for $\alpha > 60^\circ$ $V_{o(av)} = \frac{3\sqrt{3}V_m}{\pi} \cos \alpha$ $V_{o(av)}$ is same as that with R-load.
7.	1 ϕ dual converter	RL	$V_{o1(av)} = \frac{2V_m}{\pi} \cos \alpha_1$ $V_{o2(av)} = \frac{2V_m}{\pi} \cos \alpha_2$ $\alpha_1 + \alpha_2 = 180^\circ$ $i_{cir} = \frac{2V_m}{\omega L_r} [\cos \omega t - \cos \alpha_1]$