

**SOLVED PROBLEMS**

**Problem 1.1.** For network shown in figure 1.17 draw the graph, from that find  $A'$ ,  $A$ ,  $B'$ ,  $B$ ,  $C'$ ,  $C$ ,  $K$

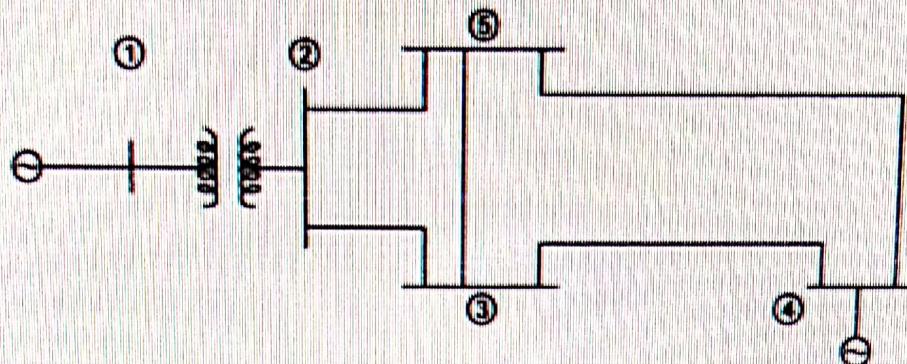


Fig. 1.17

**Sol.** For this graph

Number of Elements,  $e = 9$

Number of Nodes,  $n = 5 + 1 = 6$

Number of Branches,  $b = 5$

Number of Links,  $l = 4$

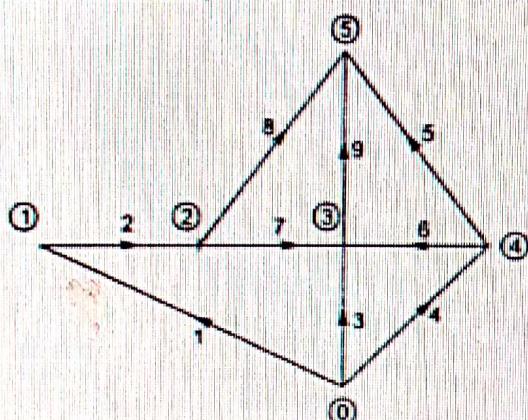


Fig. 1.17 (a) Graph

Element node incidence matrix ( $A'$ ) elements can be obtained from figure 1.17 (a) as follows :

$a_{ij} = 1$ , if the  $i^{\text{th}}$  element is incidence and oriented away from the  $j^{\text{th}}$  node.

$a_{ij} = -1$ , if the  $i^{\text{th}}$  element is incidence and oriented towards the  $j^{\text{th}}$  node.

$a_{ij} = 0$ , if the  $i^{\text{th}}$  element is not incidence to the  $j^{\text{th}}$  node.

element \ node	(0)	(1)	(2)	(3)	(4)	(5)
element	1	-1	0	0	0	0
2	0	1	-1	0	0	0
3	1	0	0	-1	0	0
4	1	0	0	0	-1	0
5	0	0	0	0	1	-1
6	0	0	0	-1	1	0
7	0	0	1	-1	0	0
8	0	0	1	0	0	-1
9	0	0	0	1	0	-1

For obtaining bus incidence matrix ( $A$ ), eliminate the reference node column in  $A'$ .

### Bus incidence matrix

element \ node	(1)	(2)	(3)	(4)	(5)	
1	-1	0	0	0	0	
2	1	-1	0	0	0	①
3	0	0	-1	0	0	
4	0	0	0	-1	0	
A = 5	0	0	0	1	-1	
6	0	0	-1	1	0	
7	0	1	-1	0	0	
8	0	1	0	0	-1	
9	0	0	1	0	-1	

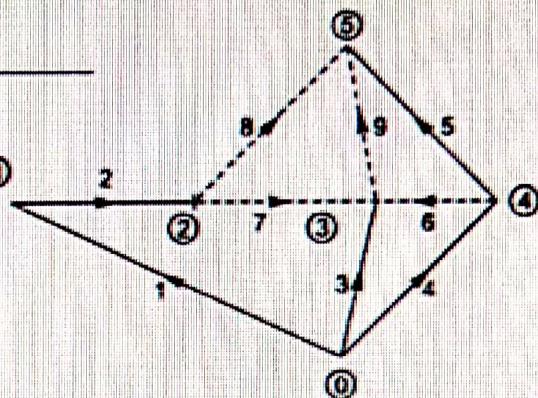


Fig. 1.17 (b) Tree

Branch path incidence matrix ( $K$ ) elements are obtained from figure. 1.17 (b).

path \ Branch	(1)	(2)	(3)	(4)	(5)	
1	-1	0	0	0	0	
2	1	-1	0	0	0	
K = 3	0	0	-1	0	0	
4	0	0	0	-1	0	
5	0	0	0	1	-1	

### Basic cut-set (B)

The elements in this matrix can be found as follows from figure. 1.17 (c)

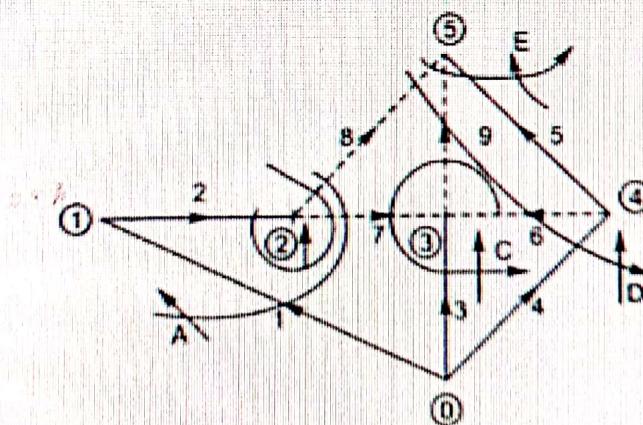


Fig. 1.17 (c) Cut-set

$B_{ij} = 1$ , if the  $i^{\text{th}}$  element is incidence to and oriented in the same direction as the  $j^{\text{th}}$  basic cut-set

$B_{ij} = -1$ , if the  $i^{\text{th}}$  element is incidence to and oriented in the opposite direction as the  $j^{\text{th}}$  basic cut-set

$B_{ij} = 0$ , if the  $i^{\text{th}}$  element is not incidence with the  $j^{\text{th}}$  basic cut-set

Branch \ Cut-set	A	B	C	D	E
1	1	0	0	0	0
2	0	1	0	0	0
3	0	0	1	0	0
4	0	0	0	1	0
$B =$	5	0	0	0	1
6	0	0	1	-1	0
7	-1	-1	1	0	0
8	-1	-1	0	1	1
9	0	0	-1	1	1

 Augmented cut-set matrix ( $B'$ )

Cut-set \ Element	A	B	C	D	E	F	G	H	I
1	1	0	0	0	0	0	0	0	0
2	0	1	0	0	0	0	0	0	0
3	0	0	1	0	0	0	0	0	0
4	0	0	0	1	0	0	0	0	0
$B' =$	5	0	0	0	1	0	0	-1	-1
6	0	0	1	-1	0	1	0	0	0
7	-1	-1	1	0	0	0	1	0	0
8	-1	-1	0	1	1	0	0	1	0
9	0	0	-1	1	1	0	0	0	1

Basic loop incidence matrix (C)

The elements can be found as follows from figure 1.17 (d)

$C_{ij} = 1$ , If the element is incidence to and oriented in the same direction as the  $j^{\text{th}}$  basic loop

$C_{ij} = -1$ , If the element is incidence to and oriented in the opposite direction as the  $j^{\text{th}}$  basic loop

$C_{ij} = 0$ , If the element is not incidence to the  $j^{\text{th}}$  basic loop

- |                   |           |
|-------------------|-----------|
| G : 1, 2, 7, 3    | 7 as link |
| I : 9, 5, 4, 7    | 9 as link |
| H : 1, 2, 8, 5, 4 | 8 as link |
| F : 3, 4, 6       | 6 as link |

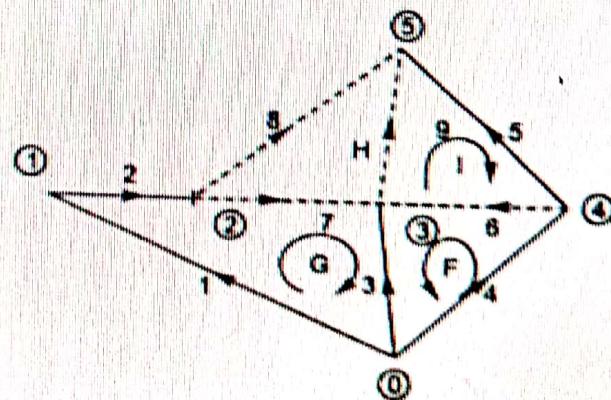


Fig. 1.17 (d)

Loop element	F	G	H	I
1	0	1	1	0
2	0	1	1	0
3	-1	-1	0	1
4	1	0	-1	-1
C = 5	0	0	-1	-1
6	1	0	0	0
7	0	1	0	0
8	0	0	1	0
9	0	0	0	1

Augmented loop incidence matrix (C') elements are obtained from figure 1.17 (d)

Loop Element	A	B	C	D	E	F	G	H	I
1	1	0	0	0	0	0	1	1	0
2	0	1	0	0	0	0	1	1	0
3	0	0	1	0	0	-1	-1	0	1
4	0	0	0	1	0	1	0	-1	-1
C' = 5	0	0	0	0	1	0	0	-1	-1
6	0	0	0	0	0	1	0	0	0
7	0	0	0	0	0	0	1	0	0
8	0	0	0	0	0	0	0	1	0
9	0	0	0	0	0	0	0	0	1

Problem 1.2. For the network shown in figure 1.18 draw the graph and tree. Also determine the 'Y<sub>bus</sub>' matrix by direct inspection method. All the mentioned values are impedances in p.u.

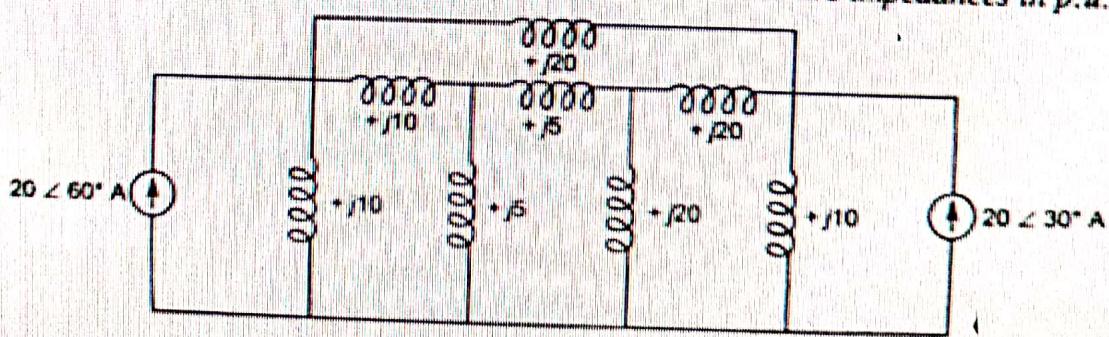


Fig. 1.18

Sol.

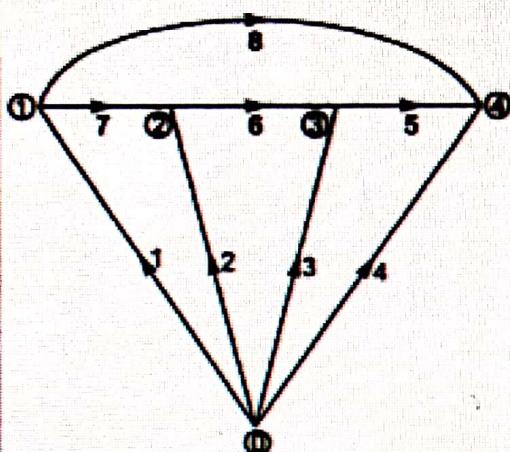


Fig. 1.19 (a) Graph

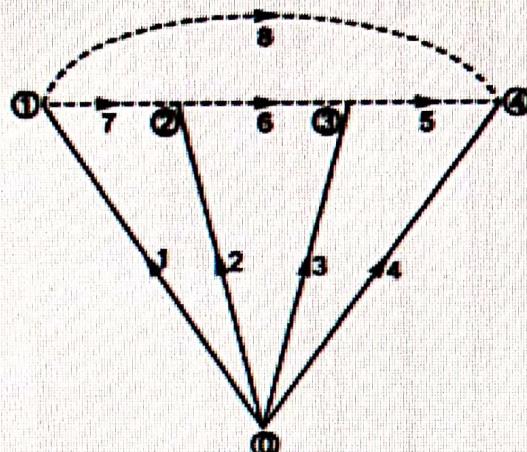


Fig. 1.19 (b) Tree

From the graph shown in figure 1.19 (a)

$$\text{Number of nodes, } n = 5$$

$$\text{Number of elements, } e = 8$$

$$\text{Number of branches, } b = n - 1 = 5 - 1 = 4$$

$$\text{Number of links, } l = e - n + 1 = 8 - 5 + 1 = 4$$

Therefore ' $Y_{\text{Bus}}$ ' has the dimension of ' $4 \times 4$ '

Given values are impedances and are given in p.u quantities. We can determine admittance values and then form the ' $Y_{\text{Bus}}$ '.

The elements of ' $Y_{\text{Bus}}$ ' can calculate as follows

$Y_{ii}$  = Sum of the admittances of the elements that are creating the node at bus 'i'

$Y_{ij}$  = Negative sign of admittance between the adjacent busses 'i' and 'j'

For  $i, j = 1, 2, 3$  and  $4$

$\therefore$  Diagonal elements :

$$Y_{11} = j0.1 + j0.1 + j0.05 = j0.25 \text{ p.u}$$

$$Y_{22} = j0.1 + j0.2 + j0.2 = j0.5 \text{ p.u}$$

$$Y_{33} = j0.1 + j0.2 + j0.05 = j0.35 \text{ p.u}$$

$$Y_{44} = j0.05 + j0.05 + j0.05 = j0.15 \text{ p.u}$$

Off-diagonal elements :

$$Y_{12} = Y_{21} = -j0.1 \text{ p.u}$$

$$Y_{13} = Y_{31} = 0.0 \text{ p.u}$$

$$Y_{14} = Y_{41} = -j0.05 \text{ p.u}$$

$$Y_{23} = Y_{32} = -j0.2 \text{ p.u}$$

$$Y_{24} = Y_{42} = 0 \text{ p.u}$$

$$Y_{34} = Y_{43} = -j0.05 \text{ p.u}$$

$$\therefore Y_{\text{Bus}} = \begin{bmatrix} j0.25 & -j0.1 & 0 & -j0.05 \\ -j0.1 & j0.5 & -j0.2 & 0 \\ 0 & -j0.2 & j0.35 & -j0.05 \\ -j0.05 & 0 & -j0.05 & j0.15 \end{bmatrix}$$

**Problem 1.3.** For problem 1.2, determine the elements of ' $Z_{\text{Loop}}$ ' by direct inspection method.

**Sol.** Here we have to replace the current sources into equivalent voltage sources when applying the direct inspection method.

The elements of loop impedance matrix as follows :

$Z_{ii}$  = Sum of the impedances of the elements forming the loop 'i'

$Z_{ij}$  = Negative sign of impedance that are common to the loops 'i' and 'j'

$\therefore$  Diagonal elements are

$$Z_{11} = +j25 \text{ p.u}$$

$$Z_{22} = +j20 \text{ p.u}$$

$$Z_{33} = +j50 \text{ p.u}$$

$$Z_{44} = +j50 \text{ p.u}$$

and off-diagonal elements are

$$Z_{12} = Z_{21} = -j5 \text{ p.u}$$

$$Z_{13} = Z_{31} = 0 \text{ p.u}$$

$$Z_{14} = Z_{41} = -j10 \text{ p.u}$$

$$Z_{23} = Z_{32} = -j10 \text{ p.u}$$

$$Z_{24} = Z_{42} = -j5 \text{ p.u}$$

$$Z_{34} = Z_{43} = -j20 \text{ p.u}$$

$$\therefore Z_{\text{Loop}} = \begin{bmatrix} +j25 & -j5 & 0 & -j10 \\ -j5 & +j20 & -j10 & -j5 \\ 0 & -j10 & +j50 & -j20 \\ -j10 & -j5 & -j20 & +j50 \end{bmatrix}$$

**Problem 1.4.** Determine the incidence matrices  $A$ ,  $B$ ,  $B'$ ,  $C$ ,  $C'$  and  $K$ . From that verify the following relations shown in figure 1.20. Take 1 as ground bus.

- (i)  $C_b = -B_i^T$   
 (iii)  $A_b K^T = U$  and

- (ii)  $C' B' T = U$   
 (iv)  $B_i = A_i K^T$

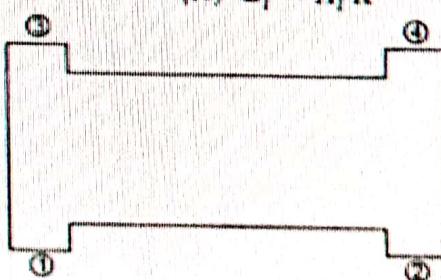


Fig. 1.20

**Sol.** Number of nodes,  $n = 4$

Number of branches,  $b = n - 1$

$$= 4 - 1 = 3$$

Number of links,

$$l = e - n + 1$$

$$= 4 - 4 + 1 = 1.$$

From figure 1.20 (b), Bus Incidence matrix [A]

$e \backslash$ bus	(2)	(3)	(4)	
1	-1	0	0	
2	0	-1	0	
3	0	1	-1	
4	1	0	-1	

$\left. \begin{array}{c} A_b \\ A_f \end{array} \right\}$

$$A_b = \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix}$$

and

$$A_f = [1 \ 0 \ -1]$$

From figure 1.20 (b), Branch path matrix (K)

branch \ path	(2)	(3)	(4)	
1	-1	0	0	
2	0	-1	-1	
3	0	0	-1	

From figure 1.20 (c), basic cut-set incidence matrix (B)

element \ cut-set	A	B	C	
1	1	0	0	
2	0	1	0	
3	0	0	1	
4	-1	1	1	

$\left. \begin{array}{c} B_b \\ B_f \end{array} \right\}$

$$B_b = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

and

$$B_f = [-1 \ 1 \ 1]$$

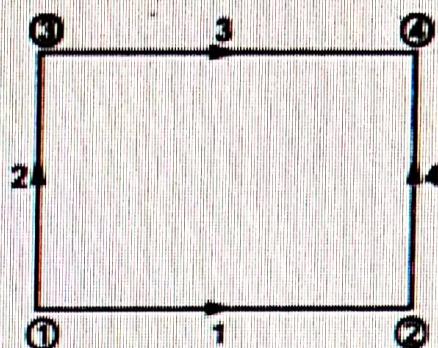


Fig. 1.20 (a) Graph

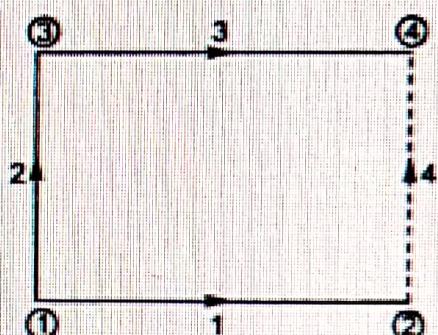


Fig. 1.20 (b) Tree

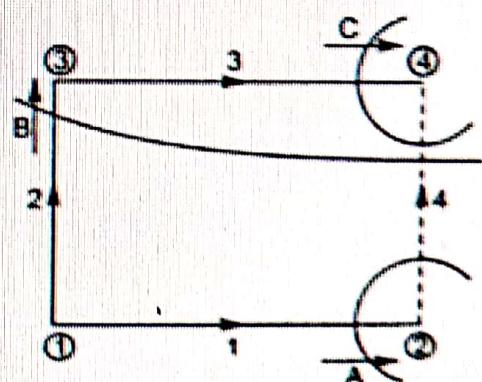


Fig. 1.20 (c)

From figure 1.20 (d). Augmented cut-set incidence matrix ( $B'$ )

element \ cut-set	A	B	C	D	
1	1	0	0	0	
2	0	1	0	0	
3	0	0	1	0	
4	-1	1	1	1	

$\therefore B'_t = [-1 \ 1 \ 1]$

and

$$U_t = [1]$$

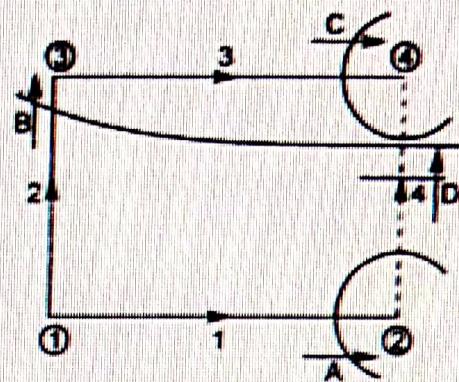


Fig. 1.20 (d)

From figure 1.20 (e), basic loop incidence matrix ( $C_b$ )

loop \ element	D	
1	1	
2	-1	
3	-1	
4	1	

$\therefore C_b = \begin{bmatrix} 1 \\ -1 \\ -1 \end{bmatrix}$

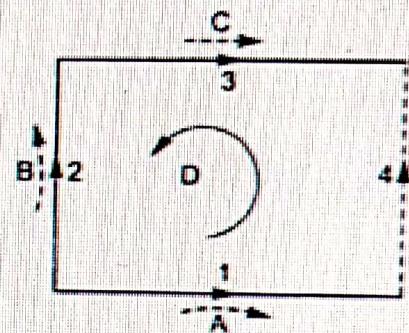


Fig. 1.20 (e)

and

$$C_l = [1]$$

From figure 1.20 (e), Augmented loop incidence matrix ( $C'$ )

loop \ element	A	B	C	D	
1	1	0	0	1	
2	0	1	0	-1	
3	0	0	1	-1	
4	0	0	0	1	

$\therefore C_b = \begin{bmatrix} 1 \\ -1 \\ -1 \end{bmatrix}$

Verification :

$$(i) C_b = -B_t^T$$

From the matrices  $C_b$  and  $B_t$  values

$$\therefore C_b = -B_t^T$$

(ii)  $C' B'^T = U$ 

$$C' = \begin{bmatrix} 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & -1 \\ 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & 1 \end{bmatrix}$$

$$B' = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ -1 & 1 & 1 & 1 \end{bmatrix}$$

$$B'^T = \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 1 \end{bmatrix}$$

$$C'(B')^T = \begin{bmatrix} 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & -1 \\ 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} = U$$

 $C'(B')^T = U$ (iii)  $A_b K^T = U$ 

$$A_b = \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix}$$

$$K = \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & -1 \\ 0 & 0 & -1 \end{bmatrix} \Rightarrow K^T = \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & -1 & -1 \end{bmatrix}$$

$$A_b \cdot K^T = \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & -1 & -1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$\therefore A_b K^T = U$$

$$(iv) B_I = A_I K^T$$

$$A_I = [1 \ 0 \ -1]$$

$$K^T = \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & -1 & -1 \end{bmatrix}$$

$$A_I K^T = [1 \ 0 \ -1] \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & -1 & -1 \end{bmatrix} = \begin{bmatrix} -1 \\ 1 \\ 1 \end{bmatrix} = B_I$$

**Problem 1.5.** For the graph shown in figure 1.21, form the necessary incidence matrices and hence verify the following relations :

$$(i) A_b K^T = U$$

$$(ii) B_I = A_I K^T$$

$$(iii) C_b = -B_I^T$$

$$(iv) C' (B')^T = U$$

**Sol.** Number of branches,  $b = n - 1$

$$\begin{aligned} b &= 4 - 1 \\ &= 3 \end{aligned}$$

$$\begin{aligned} \text{Number of links} &= e - n + 1 \\ &= 5 - 4 + 1 = 2 \end{aligned}$$

From figure 1.21, Bus incidence matrix (A)

$$A = \begin{array}{c|ccc} e \diagdown b & \textcircled{1} & \textcircled{2} & \textcircled{3} \\ \hline 1 & -1 & 0 & 0 \\ 2 & 0 & 0 & -1 \\ 4 & 1 & -1 & 0 \\ 3 & 1 & 0 & -1 \\ 5 & 0 & -1 & 1 \end{array} \left. \begin{array}{l} \} A_b \\ \} A_I \end{array} \right.$$

$$A_b = \begin{bmatrix} -1 & 0 & 0 \\ 0 & 0 & -1 \\ 1 & -1 & 0 \end{bmatrix}$$

and

$$A_I = \begin{bmatrix} 1 & 0 & -1 \\ 0 & -1 & 1 \end{bmatrix}$$

From figure 1.21 (a), branch path matrix (K)

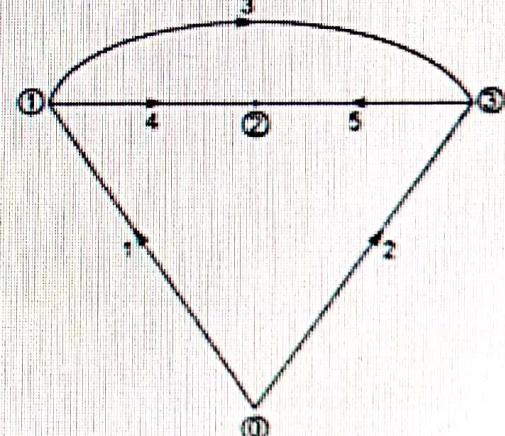


Fig. 1.21 Graph

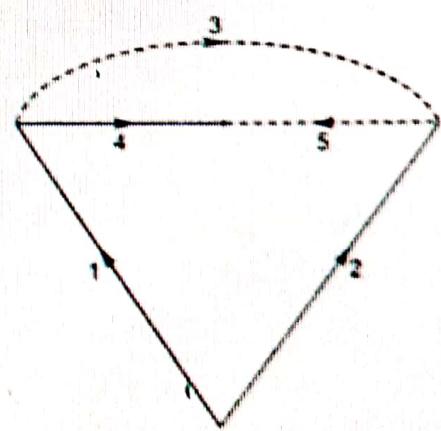


Fig. 1.21 (a) Tree

<del>b</del> path	①	②	③
1	-1	-1	0
2	0	0	-1
4	0	-1	0

$K =$

From figure 1.21 (b), basic cut-set incidence matrix ( $B$ )

<del>e</del> cut-set	A	B	C
1	1	0	0
2	0	1	0
4	0	0	1
3	-1	1	0
5	1	-1	1

$B_I = \begin{bmatrix} -1 & 1 & 0 \\ 1 & -1 & 1 \end{bmatrix}$

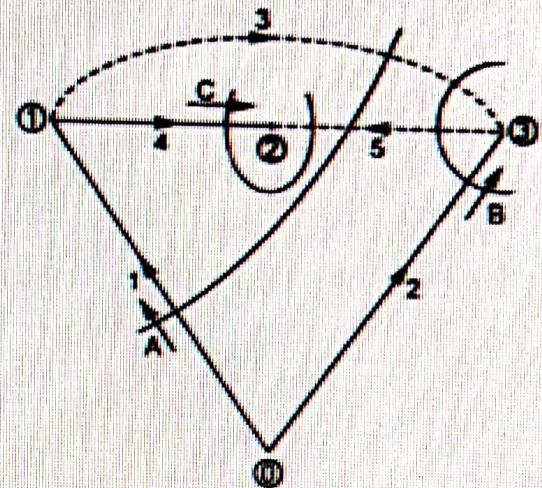


Fig. 1.21 (b)

From figure 1.21 (b), Augmented cut-set incidence matrix ( $B'$ )

<del>e</del> Cut-set	A	B	C	D	E
1	1	0	0	0	0
2	0	1	0	0	0
4	0	0	1	0	0
3	-1	1	0	1	0
5	1	-1	1	0	1

$B_I = \begin{bmatrix} -1 & 1 & 0 \\ 1 & -1 & 1 \end{bmatrix}$

$$B' = \left[ \begin{array}{ccccc|cc} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 2 & 0 & 1 & 0 & 0 & 0 & 0 \\ 4 & 0 & 0 & 1 & 0 & 0 & 0 \\ 3 & -1 & 1 & 0 & 1 & 0 & 0 \\ 5 & 1 & -1 & 1 & 0 & 1 & 0 \end{array} \right] = \left[ \begin{array}{c|cc} U_B & 0 \\ \hline B_I & U_I \end{array} \right]$$

From figure 1.21 (c), Basic loop incidence matrix ( $C$ )

<del>e</del> loop	D	E
1	1	-1
2	-1	1
4	0	-1
3	1	0
5	0	1

$C_B = \begin{bmatrix} 1 & -1 \\ -1 & 1 \\ 0 & -1 \end{bmatrix}$

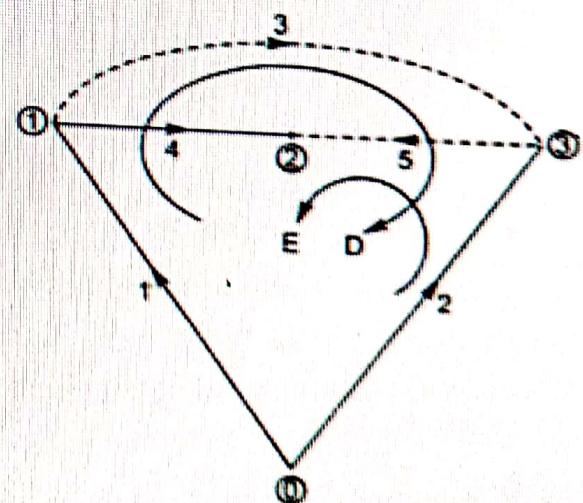


Fig. 1.21 (c)

From figure 1.21 (c), Augmented loop incidence matrix ( $C'$ )

<del>e</del> loop	A	B	C	D	E	
1	1	0	0	1	-1	
2	0	1	0	-1	1	
4	0	0	1	0	-1	$= \begin{bmatrix} U_b & C_b \\ 0 & U_I \end{bmatrix}$
3	0	0	0	1	0	
5	0	0	0	0	1	

**Verification :**

(i)  $A_b K^T = U$

$$A_b = \begin{bmatrix} -1 & 0 & 0 \\ 0 & 0 & -1 \\ 1 & -1 & 0 \end{bmatrix}$$

$$K = \begin{bmatrix} -1 & 0 & -1 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \end{bmatrix} \Rightarrow K^T = \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ -1 & 0 & -1 \end{bmatrix}$$

$$\begin{aligned} A_b \times K^T &= \begin{bmatrix} -1 & 0 & 0 \\ 0 & 0 & -1 \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ -1 & 0 & -1 \end{bmatrix} \\ &= \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = U = \text{Unit matrix.} \end{aligned}$$

(ii)  $B_I = A_I K^T$

$$\text{R.H.S. } A_I = \begin{bmatrix} 1 & 1 & -1 \\ 0 & -1 & 0 \end{bmatrix}$$

$$K^T = \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ -1 & 0 & -1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 & -1 \\ 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ -1 & 0 & -1 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 0 \\ 1 & -1 & 1 \end{bmatrix} = B_I$$

R.H.S. = L.H.S.

(iii)  $C_b = -B_I^T$

$$B_I = \begin{bmatrix} -1 & 1 & 0 \\ 1 & -1 & 1 \end{bmatrix}$$

$$-B_I^T = \begin{bmatrix} 1 & 1 \\ -1 & 1 \\ 0 & 1 \end{bmatrix} = C_b$$

$$(iv) C' (B')^T = U$$

$$C' = \begin{bmatrix} 1 & 0 & 0 & 1 & -1 \\ 0 & 1 & 0 & -1 & 1 \\ 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$(B')^T = \begin{bmatrix} 1 & 0 & 0 & -1 & 1 \\ 0 & 1 & 0 & 1 & -1 \\ 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$C'(B')^T = \begin{bmatrix} 1 & 0 & 0 & 1 & -1 \\ 0 & 1 & 0 & -1 & 1 \\ 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & -1 & 1 \\ 0 & 1 & 0 & 1 & -1 \\ 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} = U = \text{Unit matrix.}$$

**Problem 1.6.** The incidence matrix is given below. From that draw the oriented graph.

Branches

	→	1	2	3	4	5	6	7	8
nodes ↓	①	1	0	0	0	1	0	0	1
A <sup>T</sup> =	②	0	1	0	0	-1	1	0	0
	③	0	0	1	0	0	-1	1	-1
	④	0	0	0	1	0	0	-1	0

Sol.

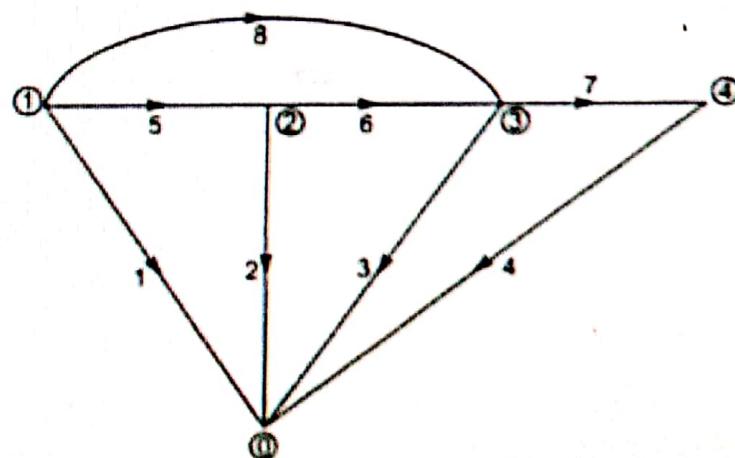


Fig. 1.22

**Problem 1.7.** For figure 1.23, the impedance data is given in table 1.1. All the impedance values are in p.u. Values. Determine  $Y_{bus}$  matrices by Singular Transformation method.

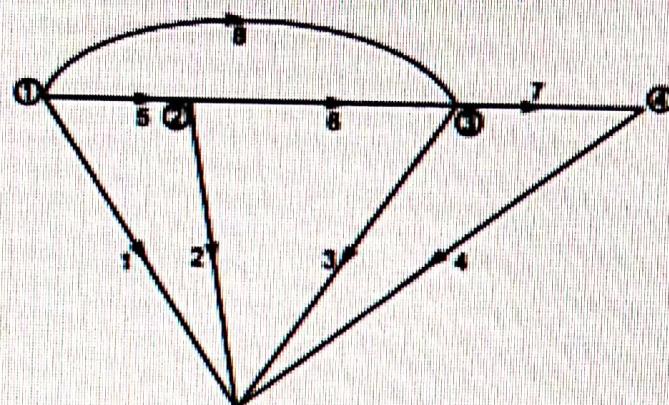


Fig. 1.23

Table 1.1

Element	Bus Code	Self Impedance In p.u
1	0 - 1	0.1
2	0 - 2	0.2
3	0 - 3	0.25
4	0 - 4	0.5
5	1 - 2	0.1
6	2 - 3	0.4
7	3 - 4	0.3
8	1 - 3	0.6

**Sol.** From figure 1.23, the Bus incidence matrix A is

$$A = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & -1 \\ 1 & 0 & -1 & 0 \end{bmatrix}$$

Primitive impedance matrix is

$$\xrightarrow{\downarrow \text{elements}} \begin{array}{cccccccc} & 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{array}$$

$$z = \begin{array}{|c|cccccccc|} \hline & 0.1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0.2 & 0 & 0 & 0 & 0 & 0 & 0 \\ 2 & 0 & 0 & 0.25 & 0 & 0 & 0 & 0 & 0 \\ 3 & 0 & 0 & 0 & 0.5 & 0 & 0 & 0 & 0 \\ 4 & 0 & 0 & 0 & 0 & 0.1 & 0 & 0 & 0 \\ 5 & 0 & 0 & 0 & 0 & 0 & 0.4 & 0 & 0 \\ 6 & 0 & 0 & 0 & 0 & 0 & 0 & 0.3 & 0 \\ 7 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 8 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0.6 \end{array}$$

Primitive admittance is given by

$$y = [z]^{-1}$$

$$y = \begin{bmatrix} 0.1 & 0 & 0 \\ 0 & 0.2 & 0 \\ 0 & 0 & 0.25 \\ 0 & 0 & 0 & 0.5 \\ 0 & 0 & 0 & 0 & 0.1 \\ 0 & 0 & 0 & 0 & 0 & 0.4 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0.3 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0.6 \end{bmatrix}^{-1}$$

∴

$$y = \begin{bmatrix} 10 \\ 0.5 \\ 0.04 \\ 0.002 \\ 0.00010 \\ 0.000025 \\ 0.0000067 \\ 0.00000333 \end{bmatrix}$$

$$Y_{\text{Bus}} = [A^T] [y] [A]$$

$$[y] [A] = \begin{bmatrix} 10 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0.5 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0.04 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0.002 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0.00010 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0.000025 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0.0000067 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0.00000333 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & -1 \\ 1 & 0 & -1 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} 10 & 0 & 0 & 0 \\ 0 & 5 & 0 & 0 \\ 0 & 0 & 4 & 0 \\ 0 & 0 & 0 & 2 \\ 10 & -10 & 0 & 0 \\ 0 & +2.5 & -2.5 & 0 \\ 0 & 0 & 6.67 & -6.67 \\ +3.33 & 0 & -3.33 & 0 \end{bmatrix}$$

$$\begin{aligned}
 [\mathbf{A}^T] [\mathbf{y}] [\mathbf{A}] &= \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} 10 & 0 & 0 & 0 \\ 0 & 5 & 0 & 0 \\ 0 & 0 & 4 & 0 \\ 0 & 0 & 0 & 2 \\ 10 & -10 & 0 & 0 \\ 0 & 2.5 & -2.5 & 0 \\ 0 & 0 & 6.67 & -6.67 \\ 3.33 & 0 & -3.33 & 0 \end{bmatrix} \\
 &= \begin{bmatrix} (10 + 10 + 3.33) & -10 & -3.33 & 0 \\ -10 & (5 + 10 + 2.5) & -2.5 & 0 \\ -3.33 & -2.5 & (4 + 2.5 + 6.67 + 3.33) & -6.67 \\ 0 & 0 & -6.67 & (2 + 6.67) \end{bmatrix} \\
 \therefore \mathbf{Y}_{\text{Bus}} &= \begin{bmatrix} 20.33 & -10 & -3.33 & 0 \\ -10 & 17.5 & -2.5 & 0 \\ -3.33 & -2.5 & 16.5 & -6.67 \\ 0 & 0 & -6.67 & 8.67 \end{bmatrix}
 \end{aligned}$$

**Problem 1.8.** For the system shown in figure 1.24, construct  $\mathbf{Y}_{\text{Bus}}$  by singular transformation method. The parameters of various elements are given in table 1.2. Take node '6' as reference node.

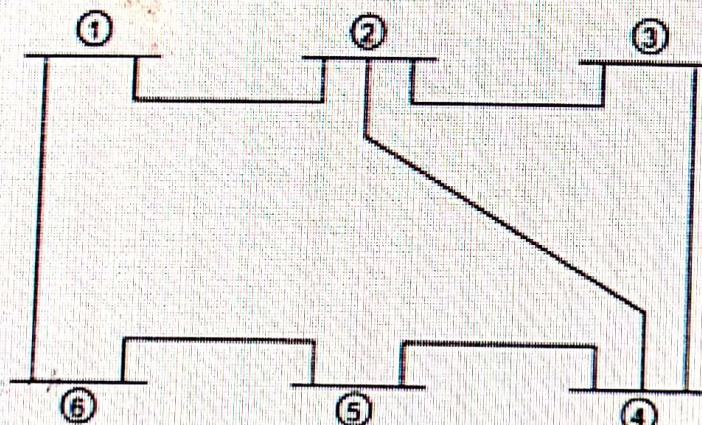


Fig. 1.24

Table 1.2

Element	Reactances in p.u
1 – 2	0.04
1 – 6	0.02
2 – 4	0.03
2 – 3	0.02
3 – 4	0.08
4 – 5	0.06
5 – 6	0.05

Sol.

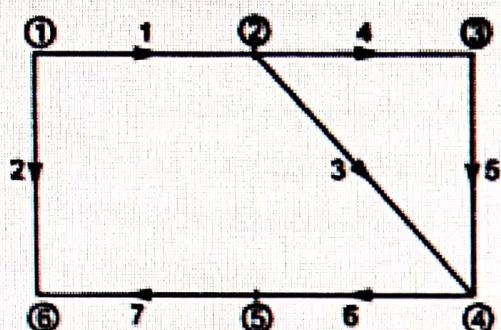


Fig. 1.24 (a) Oriented graph

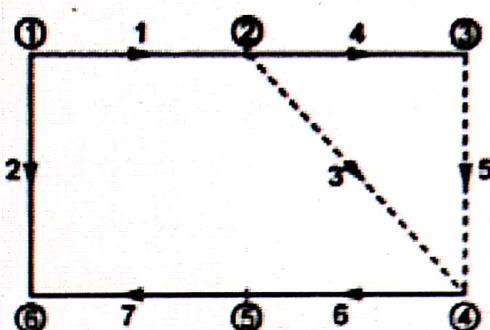


Fig. 1.24 (b) Tree

Element node incidence matrix ( $A'$ )

$e \backslash n$	(1)	(2)	(3)	(4)	(5)	(6)
1	1	-1	0	0	0	0
2	1	0	0	0	0	-1
3	0	1	0	-1	0	0
4	0	1	-1	0	0	0
5	0	0	1	-1	0	0
6	0	0	0	1	-1	0
7	0	0	0	0	1	-1

From the element node incidence matrix bus incidence matrix can be determined, i.e., by deleting the row corresponding to reference node (6).

Bus incidence matrix

$e \backslash n$	(1)	(2)	(3)	(4)	(5)
1	1	-1	0	0	0
2	1	0	0	0	0
3	0	1	0	-1	0
4	0	1	-1	0	0
5	0	0	1	-1	0
6	0	0	0	1	-1
7	0	0	0	0	1

The bus incidence matrix ( $A$ ) is rearranged by separating branches and links as follows :

$e \backslash n$	(1)	(2)	(3)	(4)	(5)	
1	1	-1	0	0	0	
2	1	0	0	0	0	
4	0	1	-1	0	0	
6	0	0	0	1	-1	
7	0	0	0	0	1	
3	0	-1	0	-1	0	$A_b$ (Branch)
5	0	0	1	-1	0	$A_t$ (Link)

Primitive impedance matrix is

$$z = \begin{bmatrix} j0.04 & & & & & & \\ 0 & j0.06 & & & & & \\ 0 & 0 & j0.03 & & & & \\ 0 & 0 & 0 & j0.02 & & & \\ 0 & 0 & 0 & 0 & j0.08 & & \\ 0 & 0 & 0 & 0 & 0 & j0.06 & \\ 0 & 0 & 0 & 0 & 0 & 0 & j0.05 \end{bmatrix}$$

Primitive admittance matrix is

$$y = [z]^{-1}$$

$$y = \begin{bmatrix} -j25 & & & & & & \\ 0 & -j16.67 & & & & & \\ 0 & 0 & -j33.39 & & & & \\ 0 & 0 & 0 & -j50 & & & \\ 0 & 0 & 0 & 0 & -j12.5 & & \\ 0 & 0 & 0 & 0 & 0 & -j16.67 & \\ 0 & 0 & 0 & 0 & 0 & 0 & -j20 \end{bmatrix}$$

$$Y_{\text{Bus}} = [A^T] [y] [A]$$

$$[A]^T [y] = -j \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ -1 & 0 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 25 \\ 0 & 16.67 \\ 0 & 0 & 33.33 \\ 0 & 0 & 0 & 50 \\ 0 & 0 & 0 & 0 & 12.5 \\ 0 & 0 & 0 & 0 & 0 & 16.67 \\ 0 & 0 & 0 & 0 & 0 & 0 & 20 \end{bmatrix}$$

$$= -j \begin{bmatrix} 25 & 16.67 & 0 & 0 & 0 & 0 & 0 \\ -25 & 0 & 33.33 & 50 & 0 & 0 & 0 \\ 0 & 0 & 0 & -50 & 12.5 & 0 & 0 \\ 0 & 0 & -33.33 & 0 & -12.5 & 16.67 & 0 \\ 0 & 0 & 0 & 0 & 0 & -16.67 & 20 \end{bmatrix}$$

$$[A^T] [y] [A] = -j \begin{bmatrix} 25 & 16.67 & 0 & 0 & 0 & 0 & 0 \\ -25 & 0 & 33.33 & 50 & 0 & 0 & 0 \\ 0 & 0 & 0 & -50 & 12.5 & 0 & 0 \\ 0 & 0 & -33.33 & 0 & -12.5 & 16.67 & 0 \\ 0 & 0 & 0 & 0 & 0 & -16.67 & 20 \end{bmatrix} \begin{bmatrix} 1 & -1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & -1 & 0 \\ 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$Y_{\text{Bus}} = -j \begin{bmatrix} (25 + 16.67) & -25 & 0 & 0 & 0 \\ -25 & (25 + 33.33 + 50) & 0 & 0 & 0 \\ 0 & -50 & (50 + 12.5) & 0 & 0 \\ 0 & -33.33 & -12.5 & (33.33 + 12.5 + 16.67) & -16.67 \\ 0 & 0 & 0 & -16.67 & (16.67 + 20) \end{bmatrix}$$

$$\therefore Y_{\text{Bus}} = -j \begin{bmatrix} 41.67 & -25 & 0 & 0 & 0 \\ -25 & 108.33 & -50 & -33.33 & 0 \\ 0 & -50 & 62.5 & -12.5 & 0 \\ 0 & -33.33 & -12.5 & 62.5 & -16.67 \\ 0 & 0 & 0 & -16.67 & 36.67 \end{bmatrix}$$

**Problem 1.9.** Determine the  $Y_{\text{Bus}}$  matrix by singular transformation method for the network shown in figure 1.25. The parameters are given in table 1.3.

Table 1.3

Element	Self Impedance in p.u		Mutual Impedance in p.u	
	Bus Code $p - q$	Impedance $Z_{pq} - pq$	Bus Code $r - s$	Impedance $Z_{pq} - rs$
1	1 - 2 (1)	0.2	—	—
2	1 - 3	0.4	1-2 (1)	0.05
3	3 - 4	0.5	—	—
4	1 - 2 (2)	0.25	1-2 (1)	0.1
5	2 - 4	0.2	—	—

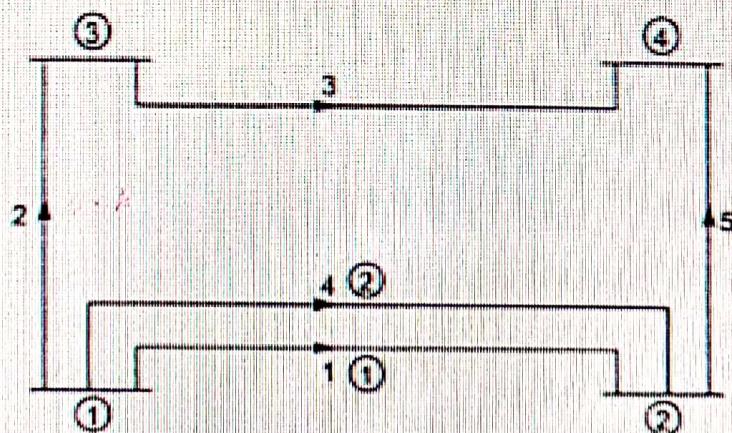


Fig. 1.25

**Sol.** Number of elements,  $e = 5$

Number of busses  $b = n - 1 = 4 - 1 = 3$

Number of links,  $l = e - n + 1 = 5 - 4 + 1 = 2$

**Element-node incidence matrix ( $A'$ )**

$e \setminus n$	①	②	③	④
1	1	-1	0	0
2	1	0	-1	0
$A' =$	3	0	1	-1
	4	1	-1	0
	5	0	1	-1

**Bus-incidence matrix ( $A$ )**

$$A = \begin{array}{c|ccc}
e \setminus n & ② & ③ & ④ \\
\hline
1 & -1 & 0 & 0 \\
2 & 0 & -1 & 0 \\
3 & 0 & 1 & -1 \\
4 & -1 & 0 & 0 \\
5 & 1 & 0 & -1
\end{array} \quad (\because ① \text{ is reference node})$$

$$A = \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 0 \\ 1 & 0 & -1 \end{bmatrix}$$

**Primitive impedance matrix [ $z$ ]**

$$z = \begin{array}{c|ccccc}
e/e & 1 & 2 & 3 & 4 & 5 \\
\hline
1 & 0.2 & 0.05 & 0 & 0.1 & 0 \\
2 & 0.05 & 0.4 & 0 & 0 & 0 \\
3 & 0 & 0 & 0.5 & 0 & 0 \\
4 & 0.1 & 0 & 0 & 0.25 & 0 \\
5 & 0 & 0 & 0 & 0 & 0.02
\end{array}$$

**Primitive admittance matrix  $y = [z]^{-1}$**

$$y = [z]^{-1} = \begin{bmatrix} 0.2 & 0.05 & 0 & 0.1 & 0 \\ 0.05 & 0.4 & 0 & 0 & 0 \\ 0 & 0 & 0.5 & 0 & 0 \\ 0.1 & 0 & 0 & 0.25 & 0 \\ 0 & 0 & 0 & 0 & 0.02 \end{bmatrix}^{-1}$$

To calculate  $z^{-1}$  there are two methods :

**Method 1 :**

$$y = [z]^{-1} = \begin{bmatrix} 0.2 & 0.05 & 0 & 0.1 & 0 \\ 0.05 & 0.4 & 0 & 0 & 0 \\ 0 & 0 & 0.5 & 0 & 0 \\ 0.1 & 0 & 0 & 0.25 & 0 \\ 0 & 0 & 0 & 0 & 0.02 \end{bmatrix}^{-1}$$

**Step 1. Interchange row 3 and 4**

$$\mathbf{y}' = \begin{bmatrix} 0.2 & 0.05 & 0 & 0.1 & 0 \\ 0.05 & 0.4 & 0 & 0 & 0 \\ 0.1 & 0 & 0 & 0.25 & 0 \\ 0 & 0 & 0.5 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0.2 \end{bmatrix}^{-1}$$

**Step 2. Interchange column 3 and 4**

$$\mathbf{y}'' = \begin{bmatrix} 0.2 & 0.05 & 0.1 & 0 & 0 \\ 0.05 & 0.4 & 0 & 0 & 0 \\ 0.1 & 0 & 0.25 & 0 & 0 \\ 0 & 0 & 0 & 0.5 & 0 \\ 0 & 0 & 0 & 0 & 0.2 \end{bmatrix}^{-1} = \begin{bmatrix} \mathbf{A}_1 & \mathbf{A}_2 \\ \mathbf{A}_3 & \mathbf{A}_4 \end{bmatrix}$$

**Step 3. Above matrix can divide into 4 submatrices**

$$\mathbf{A}_1 = \begin{bmatrix} 0.2 & 0.05 & 0.1 \\ 0.05 & 0.4 & 0 \\ 0.1 & 0 & 0.25 \end{bmatrix}$$

$$\mathbf{A}_2 = \begin{bmatrix} 0 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \quad \mathbf{A}_3 = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$\mathbf{A}_4 = \begin{bmatrix} 0.5 & 0 \\ 0 & 0.2 \end{bmatrix}$$

$$\mathbf{A}_1^{-1} = \begin{bmatrix} 6.5 & -0.81 & -2.6 \\ -0.81 & 2.6 & 0.33 \\ -2.6 & 0.33 & 5.0 \end{bmatrix}$$

$$\mathbf{A}_4^{-1} = \begin{bmatrix} 2 & 0 \\ 0 & 5 \end{bmatrix}$$

**Step 4.**

$$\mathbf{y}'' = \begin{bmatrix} \mathbf{A}_1^{-1} & \mathbf{A}_2 \\ \mathbf{A}_3 & \mathbf{A}_4^{-1} \end{bmatrix}$$

$$\mathbf{y}'' = \begin{bmatrix} 6.5 & -0.81 & -2.6 & 0 & 0 \\ -0.81 & 2.6 & 0.33 & 0 & 0 \\ -2.6 & 0.33 & 5 & 0 & 0 \\ 0 & 0 & 0 & 2 & 0 \\ 0 & 0 & 0 & 0 & 5 \end{bmatrix}$$

**Step 5. Interchange column 3 and 4**

$$y' = \begin{bmatrix} 6.5 & -0.81 & 0 & -2.6 & 0 \\ -0.81 & 2.6 & 0 & 0.33 & 0 \\ -2.6 & 0.33 & 0 & 5 & 0 \\ 0 & 0 & 2 & 0 & 0 \\ 0 & 0 & 0 & 0 & 5 \end{bmatrix}$$

**Step 6. Interchange row 3 and 4**

$$y = [z^{-1}] = \begin{bmatrix} 6.5 & -0.81 & 0 & -2.6 & 0 \\ 0.81 & 2.6 & 0 & 0.33 & 0 \\ 0 & 0 & 2 & 0 & 0 \\ -2.6 & 0.33 & 0 & 5 & 0 \\ 0 & 0 & 0 & 0 & 5 \end{bmatrix}$$

**Limitations :** This method is applicable only the matrices  $A_2$  and  $A_3$  are having the elements zero's only. Otherwise it is not applicable.

**Method 2 :**

$$y = [z^{-1}] = \begin{bmatrix} 0.2 & 0.05 & 0 & 0.1 & 0 \\ 0.05 & 0.4 & 0 & 0 & 0 \\ 0 & 0 & 0.5 & 0 & 0 \\ 0.1 & 0 & 0 & 0.25 & 0 \\ 0 & 0 & 0 & 0 & 0.2 \end{bmatrix}^{-1} = \begin{bmatrix} A_1 & A_2 \\ A_3 & A_4 \end{bmatrix}^{-1}$$

Let

$$\begin{bmatrix} A_1 & A_2 \\ A_3 & A_4 \end{bmatrix}^{-1} = \begin{bmatrix} B_1 & B_2 \\ B_3 & B_4 \end{bmatrix}$$

The values of matrices  $B_1$ ,  $B_2$ ,  $B_3$  and  $B_4$  are

$$B_1 = [A_1 - (A_2 A_4^{-1} A_3)]^{-1}$$

$$A_4^{-1} = \begin{bmatrix} 0.25 & 0 \\ 0 & 0.2 \end{bmatrix}^{-1} = \begin{bmatrix} 4 & 0 \\ 0 & 5 \end{bmatrix}$$

$$A_2 = \begin{bmatrix} 0.1 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix}$$

$$A_3 = \begin{bmatrix} 0.1 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$A_2 A_4^{-1} A_3 = \begin{bmatrix} 0.1 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} 4 & 0 \\ 0 & 5 \end{bmatrix} \begin{bmatrix} 0.1 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} 0.4 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} 0.1 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} 0.04 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$[A_1 - (A_2 A_4^{-1} A_3)]^{-1} = \left\{ \begin{bmatrix} 0.2 & 0.05 & 0 \\ 0.05 & 0.4 & 0 \\ 0 & 0 & 0.5 \end{bmatrix} - \begin{bmatrix} 0.04 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \right\}^{-1}$$

$$= \begin{bmatrix} 0.16 & 0.05 & 0 \\ 0.05 & 0.4 & 0 \\ 0 & 0 & 0.5 \end{bmatrix}^{-1}$$

$$B_1 = \begin{bmatrix} 6.5 & -0.81 & 0 \\ -0.81 & 2.6 & 0 \\ 0 & 0 & 2 \end{bmatrix}$$

$$B_2 = -B_1 A_2 A_4^{-1}$$

$$= \begin{bmatrix} -6.5 & 0.81 & 0 \\ 0.81 & -2.6 & 0 \\ 0 & 0 & -2 \end{bmatrix} \begin{bmatrix} 0.1 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} 4 & 0 \\ 0 & 5 \end{bmatrix}$$

$$= \begin{bmatrix} -6.5 & 0.81 & 0 \\ 0.81 & -2.6 & 0 \\ 0 & 0 & -2 \end{bmatrix} \begin{bmatrix} 0.4 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix}$$

$$B_2 = \begin{bmatrix} -2.6 & 0 \\ 0.324 & 0 \\ 0 & 0 \end{bmatrix}$$

$$B_3 = B_2^T = \begin{bmatrix} -2.6 & 0.324 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$B_4 = A_4^{-1} - (A_4^{-1} A_3 B_2)$$

$$A_4^{-1} A_3 B_2 = \begin{bmatrix} 4 & 0 \\ 0 & 5 \end{bmatrix} \begin{bmatrix} 0.1 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} -2.6 & 0 \\ 0.324 & 0 \\ 0 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} 0.4 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} -2.6 & 0 \\ 0.324 & 0 \\ 0 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} -1.04 & 0 \\ 0 & 0 \end{bmatrix}$$

$$\mathbf{B}_4 = \mathbf{A}_4^{-1} - (\mathbf{A}_4^{-1} \mathbf{A}_3 \mathbf{B}_2)$$

$$= \begin{bmatrix} 4 & 0 \\ 0 & 5 \end{bmatrix} - \begin{bmatrix} -1.04 & 0 \\ 0 & 0 \end{bmatrix} = \begin{bmatrix} 5.04 & 0 \\ 0 & 5 \end{bmatrix}$$

$$\therefore \mathbf{y} = \mathbf{z}^{-1} = \begin{bmatrix} \mathbf{B}_1 & \mathbf{B}_2 \\ \mathbf{B}_3 & \mathbf{B}_4 \end{bmatrix} = \begin{bmatrix} 6.5 & -0.81 & 0 & -2.6 & 0 \\ -0.81 & 2.6 & 0 & 0.324 & 0 \\ 0 & 0 & 2 & 0 & 0 \\ -2.6 & 0.324 & 0 & 5.04 & 0 \\ 0 & 0 & 0 & 0 & 5 \end{bmatrix}$$

Next after calculating primitive admittance matrix.

$$\mathbf{Y}_{\text{Bus}} = [\mathbf{A}^T] [\mathbf{y}] [\mathbf{A}]$$

$$\mathbf{Y}_{\text{Bus}} = \begin{bmatrix} -1 & 0 & 0 & -1 & 1 \\ 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 \end{bmatrix} \begin{bmatrix} 0.6 & -0.81 & 0 & -2.6 & 0 \\ -0.81 & 2.6 & 0 & 0.33 & 0 \\ 0 & 0 & 2 & 0 & 0 \\ -2.6 & 0.33 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 5 \end{bmatrix} \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 0 \\ 1 & 0 & -1 \end{bmatrix}$$

$$= \begin{bmatrix} -0.6 + 2.6 & 0.81 - 0.33 & 0 & 2.6 & 5 \\ 0.81 & -2.6 & 2 & -0.33 & 0 \\ 0 & 0 & -2 & 0 & -5 \end{bmatrix} \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 0 \\ 1 & 0 & -1 \end{bmatrix}$$

$$= \begin{bmatrix} 2 & 0.48 & 0 & 2.6 & 5 \\ 0.81 & -2.6 & 2 & -0.33 & 0 \\ 0 & 0 & -2 & 0 & -5 \end{bmatrix} \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 0 \\ 1 & 0 & -1 \end{bmatrix}$$

$$\mathbf{Y}_{\text{Bus}} = \begin{bmatrix} 0.4 & -0.48 & -5 \\ -0.48 & 4.6 & -2 \\ -5 & -2 & 7 \end{bmatrix}$$

$$\mathbf{Z}_{\text{Bus}} = [\mathbf{Y}_{\text{Bus}}]^{-1} = \{[\mathbf{A}^T] [\mathbf{y}] [\mathbf{A}]\}^{-1}$$

$$= \begin{bmatrix} 0.4 & -0.48 & -5 \\ -0.48 & 4.6 & -2 \\ -5 & -2 & 7 \end{bmatrix}$$

$$\mathbf{Z}_{\text{Bus}} = \begin{bmatrix} -0.25 & -0.116 & -0.208 \\ -0.116 & -0.193 & -0.028 \\ -0.208 & -0.028 & -0.014 \end{bmatrix}$$

**Problem 1.10.** Determine  $\mathbf{Y}_{\text{bus}}$  matrix for problem 1.7 by direct inspection method.

**Sol.**

**Diagonal elements**

$$Y_{11} = \frac{1}{0.1} + \frac{1}{0.1} + \frac{1}{0.5} = 10 + 10 + 1.67 = 21.67$$

$$Y_{22} = \frac{1}{0.2} + \frac{1}{0.1} + \frac{1}{0.4} = 5 + 10 + 2.5 = 17.5$$

$$Y_{33} = \frac{1}{0.25} + \frac{1}{0.4} + \frac{1}{0.3} = 4 + 2.5 + 3.33 = 9.83$$

$$Y_{44} = \frac{1}{0.5} + \frac{1}{0.3} = 2 + 3.33 = 5.33.$$

**Off-diagonal elements**

$$Y_{12} = Y_{21} = -\frac{1}{0.1} = -10$$

$$Y_{13} = Y_{31} = -\frac{1}{0.5} = -1.67$$

$$Y_{14} = Y_{41} = 0$$

$$Y_{23} = Y_{32} = -\frac{1}{0.4} = -2.5$$

$$Y_{24} = Y_{42} = 0$$

$$Y_{34} = Y_{43} = -\frac{1}{0.3} = -3.33$$

$$\mathbf{Y}_{\text{bus}} = \begin{bmatrix} 21.67 & -10 & -1.67 & 0 \\ -10 & 17.5 & -2.5 & 0 \\ -1.67 & -2.5 & 9.83 & -3.33 \\ 0 & 0 & -3.33 & 5.33 \end{bmatrix}$$

**Problem 1.11.** The network shown in figure 1.26. Draw graph and tree. Determine the  $\mathbf{Y}_{\text{bus}}$  by direct inspection method and verify  $\mathbf{Y}_{\text{bus}}$  by nodal equation analysis. The admittance values are given in p.u quantities.

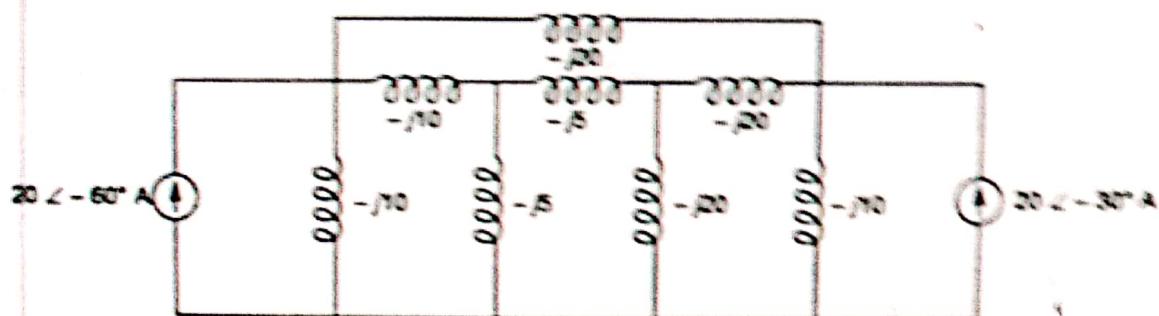


Fig. 1.26

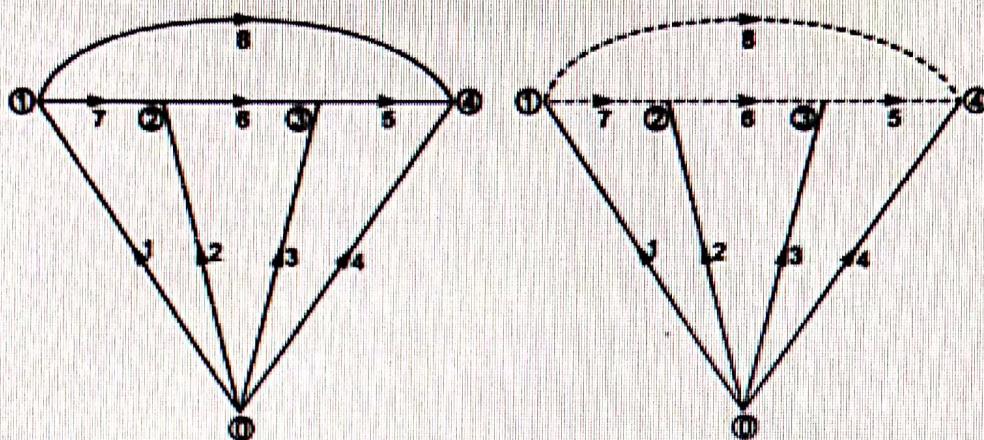
**Sol.**

Fig. 1.26 (a) Graph

Fig. 1.26 (b) Tree

**By Direct Inspection Method****Diagonal elements**

$$Y_{11} = -j10 + (-j10) + (-j20) = -j40$$

$$Y_{22} = -j5 + (-j5) + (-j10) = -j20$$

$$Y_{33} = -j5 + (-j20) + (-j20) = -j45$$

$$Y_{44} = -j20 + (-j20) + (-j10) = -j50$$

**Off-diagonal elements**

$$Y_{21} = Y_{12} = -(-j10) = +j10$$

$$Y_{13} = Y_{31} = 0$$

$$Y_{14} = Y_{41} = -(-j20) = j20$$

$$Y_{23} = Y_{32} = -(-j5) = j5$$

$$Y_{24} = Y_{42} = 0$$

$$Y_{34} = Y_{43} = -(-j20) = j20$$

$$\therefore Y_{\text{Bus}} = \begin{bmatrix} -j40 & j10 & 0 & j20 \\ j10 & -j20 & j5 & 0 \\ 0 & j5 & -j45 & j20 \\ j20 & 0 & j20 & -j50 \end{bmatrix}$$

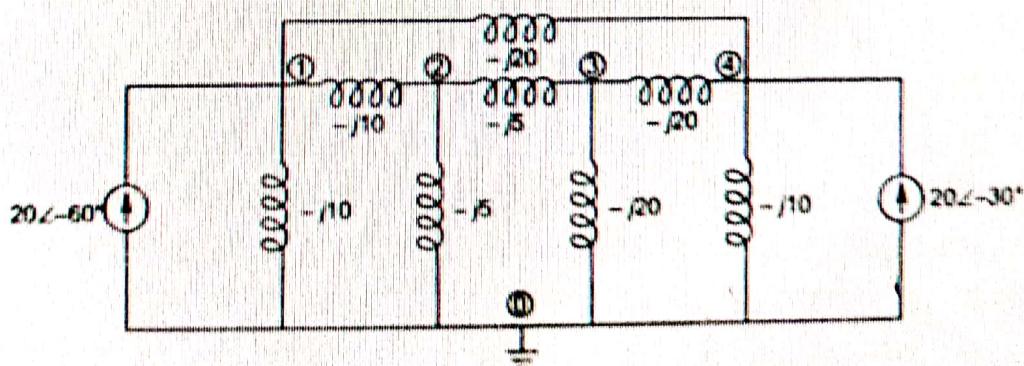
**Verification by Nodal Analysis Method**

Fig. 1.26 (c)

- Let voltages at
- node ① =  $V_1$
  - node ② =  $V_2$
  - node ③ =  $V_3$
  - node ④ =  $V_4$

Writing nodal equations for figure 1.26 (c)

At node ①

$$(V_1 - 0)(-j10) + (V_1 - V_2)(-j10) + (V_1 - V_4)(-j20) = 20 \angle -60^\circ$$

$$V_1(-j10 - j10 - j20) + V_2(j10) + V_4(j20) = 20 \angle -60^\circ$$

$$-j40 V_1 + j10 V_2 + j20 V_4 = 20 \angle -60^\circ \quad \dots(1.85)$$

At node ②

$$(V_2 - V_1)(-j10) + (V_2 - V_3)(-j5) + (V_2 - 0)(-j5) = 0$$

$$j10 V_1 + (-j10 - j5 - j5) V_2 + j5 V_3$$

$$j10 V_1 + (-j20) V_2 + j5 V_3 = 0 \quad \dots(1.86)$$

At node ③

$$(V_3 - V_2)(-j5) + (V_3 - 0)(-j20) + (V_3 - V_4)(-j20) = 0$$

$$j5 V_2 + (-j5 - j20 - j20) V_3 + j20 V_4 = 0$$

$$j5 V_2 + (-j45) V_3 + j20 V_4 = 0 \quad \dots(1.87)$$

At node ④

$$V_2(-j10) + (V_4 - V_1)(-j20) + (V_4 - V_3)(-j20) = 20 \angle -30^\circ$$

$$+ j20 V_1 + j20 V_3 + (-j10 - j20 - j20) V_4 = 20 \angle -30^\circ$$

$$+ j20 V_1 + j20 V_3 + (-j50) V_4 = 20 \angle -30^\circ \quad \dots(1.88)$$

Writing the equations (1.85), (1.86), (1.87) and (1.88) in matrix form.

$$\begin{bmatrix} 20 \angle -60^\circ \\ 0 \\ 0 \\ 20 \angle -30^\circ \end{bmatrix} = \begin{bmatrix} -j40 & j10 & 0 & j20 \\ j10 & -j20 & j5 & 0 \\ 0 & j5 & -j45 & j20 \\ j20 & 0 & j20 & -j50 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}$$

$$[I_{\text{Bus}}] = [Y_{\text{Bus}}] [V_{\text{Bus}}]$$

$$Y_{\text{Bus}} = \begin{bmatrix} -j40 & j10 & 0 & j20 \\ j10 & -j20 & j5 & 0 \\ 0 & j5 & -j45 & j20 \\ j20 & 0 & j20 & -j50 \end{bmatrix}$$