
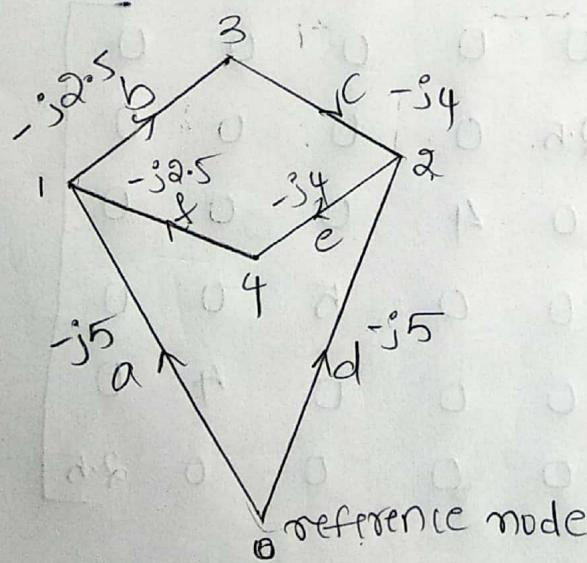
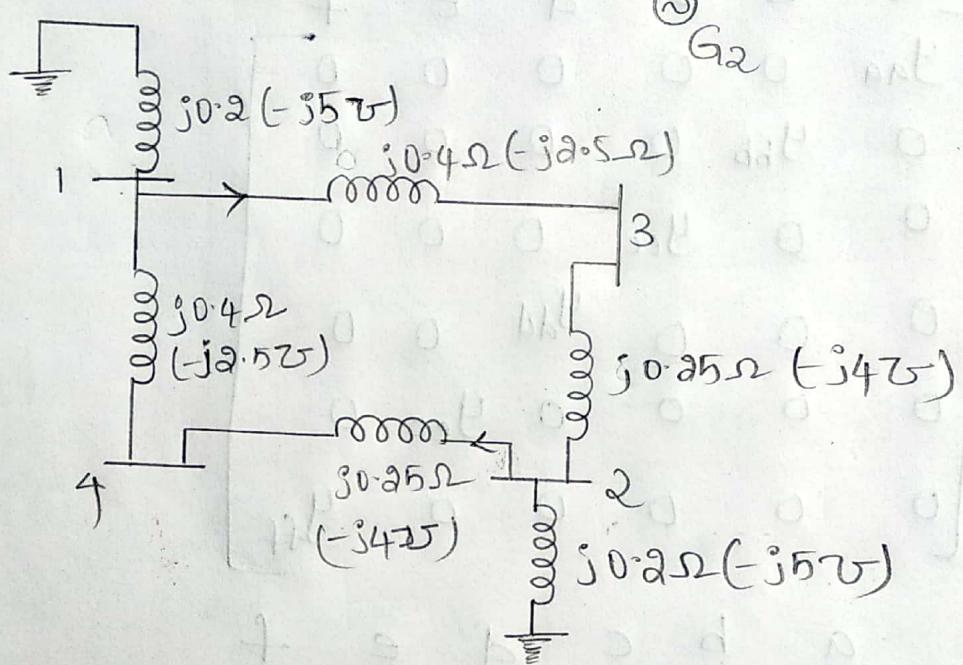


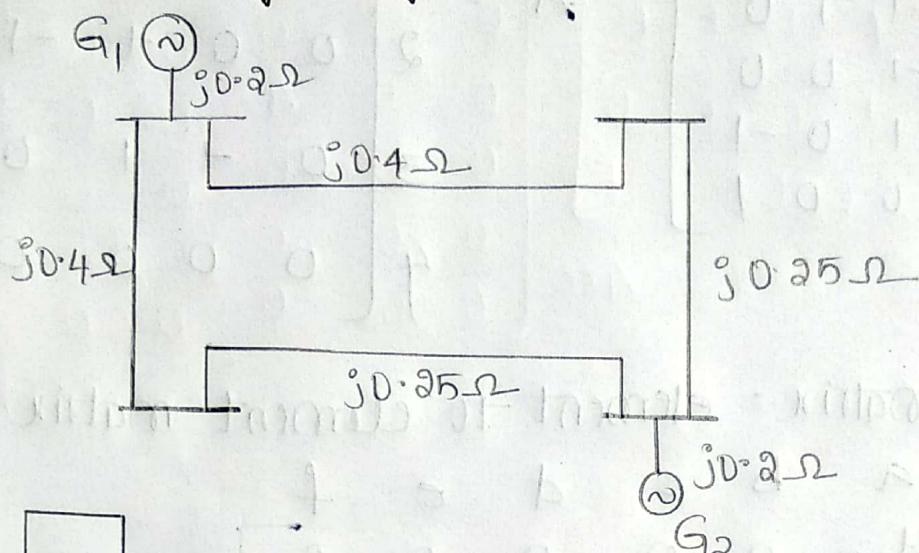* Find 4 Bus for the following Power system as shown in fig b by using singular transformation.



$$A = \begin{bmatrix} a & 1 & 2 & 3 & 4 \\ b & -1 & 0 & 0 & 0 \\ c & 1 & 0 & -1 & 0 \\ d & 0 & -1 & 1 & 0 \\ e & 0 & -1 & 0 & 0 \\ f & -1 & 0 & 0 & 1 \end{bmatrix}$$

$$A^t = \begin{bmatrix} a & b & c & d & e & f \\ 1 & -1 & 1 & 0 & 0 & 0 \\ 2 & 0 & 0 & 1 & -1 & 1 \\ 3 & 0 & -1 & 1 & 0 & 0 \\ 4 & 0 & 0 & 0 & 0 & -1 \end{bmatrix}$$

Primitive matrix = element to element matrix

$$Y = a \begin{bmatrix} a & b & c & d & e & f \\ y_{aa} & 0 & 0 & 0 & 0 & 0 \\ b & 0 & y_{bb} & 0 & 0 & 0 \\ c & 0 & 0 & y_{cc} & 0 & 0 \\ d & 0 & 0 & 0 & y_{dd} & 0 \\ e & 0 & 0 & 0 & 0 & y_{ee} \\ f & 0 & 0 & 0 & 0 & y_{ff} \end{bmatrix}$$

$$Y = -j \begin{bmatrix} a & b & c & d & e & f \\ 5 & 0 & 0 & 0 & 0 & 0 \\ b & 0 & 2.5 & 0 & 0 & 0 \\ c & 0 & 0 & 4 & 0 & 0 \\ d & 0 & 0 & 0 & 5 & 0 \\ e & 0 & 0 & 0 & 0 & 4 \\ f & 0 & 0 & 0 & 0 & 2.5 \end{bmatrix}$$

$$Y_{BUS} = [A^T] [Y] [A]$$

$$\therefore -j \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & -1 \\ 0 & 0 & -1 & -1 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix}_{4 \times 6} \begin{bmatrix} 5 & 0 & 0 & 0 & 0 & 0 \\ 0 & 2.5 & 0 & 0 & 0 & 0 \\ 0 & 0 & 4 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 4 & 0 \\ 0 & 0 & 0 & 0 & 0 & 2.5 \end{bmatrix}_{6 \times 6}$$

$$\begin{bmatrix} -1 & 0 & 0 & 0 \\ 1 & 0 & -1 & 0 \\ 0 & -1 & 1 & 0 \\ 0 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 \\ -1 & 0 & 0 & 1 \end{bmatrix}_{6 \times 4}$$

$$\Rightarrow [Y] [A]$$

$$\therefore \begin{bmatrix} 5x-1+0 & 0 & 0 & 0 \\ 0+2.5 & 0 & -2.5 & 0 \\ 0 & -4 & 4 & 0 \\ 0 & -5 & 0 & 0 \\ 0 & 4 & 0 & -4 \\ -2.5 & 0 & 0 & 2.5 \end{bmatrix} = \begin{bmatrix} -5 & 0 & 0 & 0 \\ 2.5 & 0 & -2.5 & 0 \\ 0 & -4 & 4 & 0 \\ 0 & -5 & 0 & 0 \\ 0 & 4 & 0 & -4 \\ -2.5 & 0 & 0 & 2.5 \end{bmatrix}$$



$$\Rightarrow [A^T] [Y] [A]$$

$$\therefore -j \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & -1 \\ 0 & 0 & -1 & -1 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} -5 & 0 & 0 & 0 \\ 2.5 & 0 & -2.5 & 0 \\ 0 & -4 & 4 & 0 \\ 0 & -5 & 0 & 0 \\ 0 & 4 & 0 & -4 \\ -2.5 & 0 & 0 & 2.5 \end{bmatrix}$$

$$= -j \begin{bmatrix} 5+2.5+2.5 & 0 & -2.5 & -2.5 \\ 0 & 4+5+4 & -4+2.5 & -4 \\ -2.5 & -4 & 2.5+4 & 0 \\ -2.5 & -4 & 0 & 4+2.5 \end{bmatrix}$$

$$\gamma_{\text{bus}} = -j \begin{bmatrix} 10 & 0 & -2.5 & -2.5 \\ 0 & 13 & -1.5 & -4 \\ 2.5 & -4 & 6.5 & 0 \\ -2.5 & -4 & 0 & 6.5 \end{bmatrix}$$

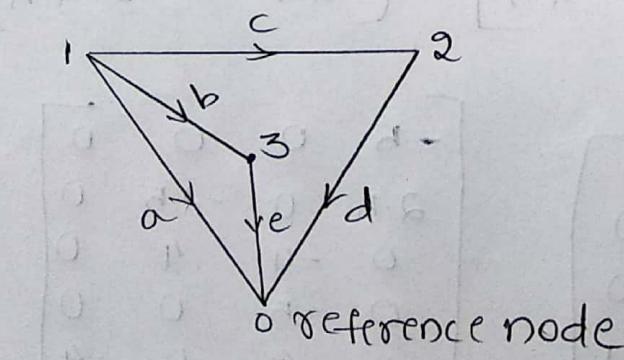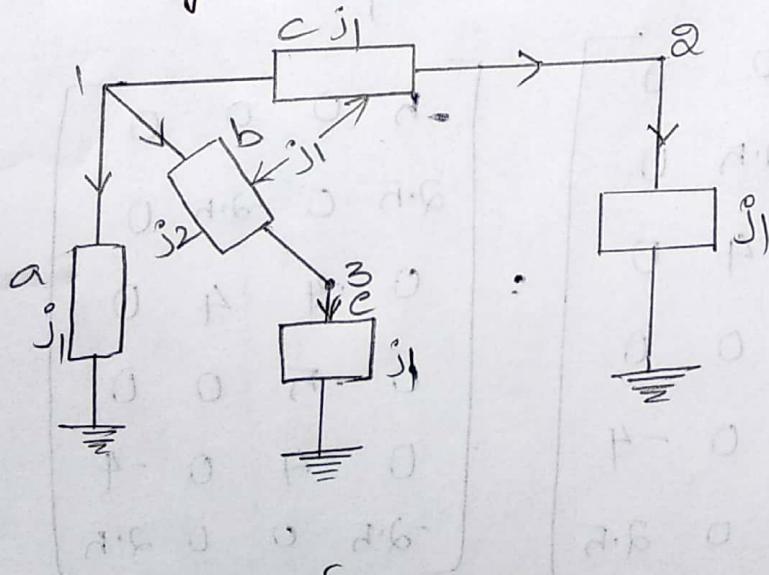* Determination primitive impedance, primitive admittance and γ_{bus} of the following interconnected system given by considering line reactances.



$$A = \begin{bmatrix} 1 & 0 & 0 \\ 1 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \quad A^t = \begin{bmatrix} 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 \\ 0 & -1 & 0 & 0 & 1 \end{bmatrix} \quad (3)$$

$$|Z| = \begin{bmatrix} a & b & c & d & e \\ z_{aa} & 0 & 0 & 0 & 0 \\ 0 & z_{bb} & z_{bc}^* & 0 & 0 \\ 0 & z_{cb}^* & z_{cc} & 0 & 0 \\ 0 & 0 & 0 & z_{dd} & 0 \\ 0 & 0 & 0 & 0 & z_{ee} \end{bmatrix}$$

$$Z = j \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 2 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} \quad \bar{z} = y = -j \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 1 & 0.5 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$Y_{BUS} = [A^t] [Y] [A]$$

$$[Y] [A] = -j \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 0.5 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 1 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$Y_{\text{BUS}} = [A^T] [Y] [A]$$


$$= -j \begin{bmatrix} 1 & 0 & 0 \\ 0.5+j & -1 & 0.5 \\ 1+j & -1 & -1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \cdot \begin{bmatrix} 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 \\ 0 & -1 & 0 & 0 & 1 \end{bmatrix}$$

$$= -j \begin{bmatrix} 1 & 1 & 1 & 0 & 0 \\ 1.5 & 0 & 2.5 & -1 & 0.5 \\ 2 & 3 & 3 & -1 & -1 \\ 0 & 0 & -1 & 1 & 0 \\ 0 & -1 & 0 & 0 & 1 \end{bmatrix}$$

* Form Y_{BUS} for the following system as shown in below diagram

Element	Bus code	Self impedance in per unit
1	0-1	0.1
2	0-2	0.2
3	0-3	0.3
4	0-4	0.35
5	1-2	0.4
6	2-3	0.1
7	3-4	0.2
8	1-3	0.15


SOL

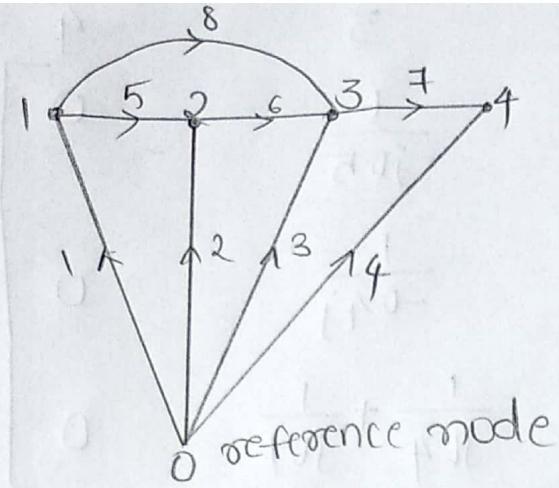


* Form Y-Tbus for the following system :
Element line reactance (impedance)

A-B	0.1Ω
A-C	0.2Ω
A-D	0.3Ω
B-C	0.4Ω
C-D	0.45Ω
B-D	0.35Ω

SOL

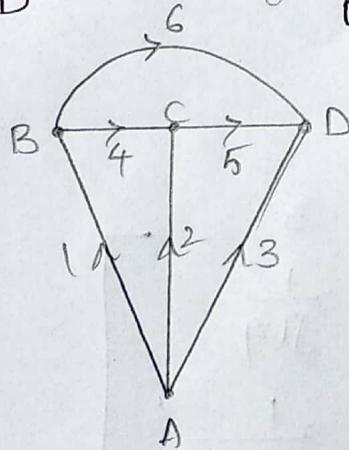


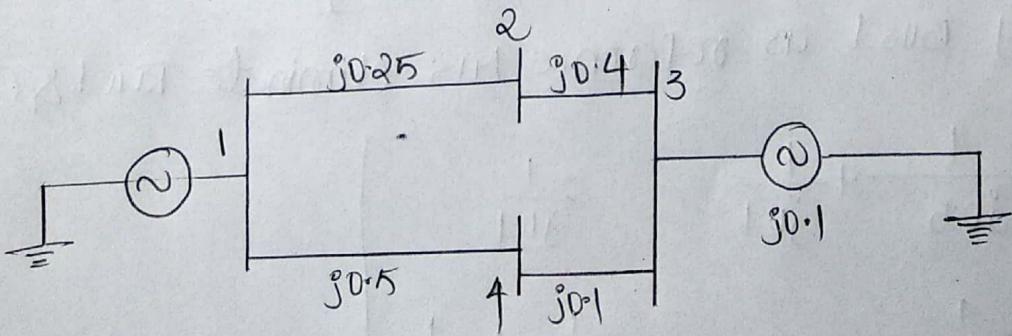* Form Y bus for the following system given below. Consider line reactance are in per unit. By direct inspection method.



$$Y_{BUS} = \begin{bmatrix} 1 & \frac{1}{j0.25} + \frac{1}{j0.5} & -\frac{1}{j0.25} & \frac{1}{-j0.5} \\ 2 & \frac{1}{-0.25} & \frac{1}{0.25} + \frac{1}{j0.4} & \frac{1}{-0.4j} \\ 3 & \frac{1}{-j0.4} & \frac{1}{-j0.1} & \frac{1}{j0.4} + \frac{1}{j0.1} \\ 4 & 0 & 0 & 0 \end{bmatrix}$$

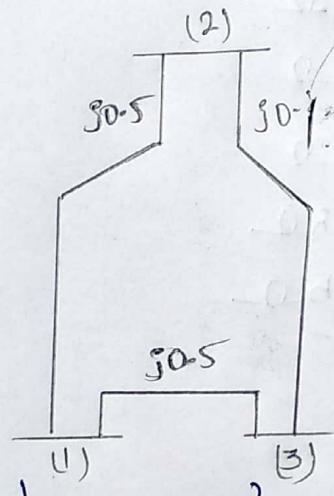* Obtain 4-bus by direct inspection method for the following given n/w take bus 1 as a reference bus and the impedance marks in per unit.




$$Y_{BUS} = \begin{bmatrix} 1 & \frac{1}{j0.3} + \frac{1}{j0.4} & -\frac{1}{j0.5} & \frac{1}{j0.4} \\ 2 & -\frac{1}{j0.5} & \frac{1}{j0.5} + \frac{1}{j0.1} & \frac{1}{j0.1} \\ 3 & \frac{1}{j0.4} & -\frac{1}{j0.1} & \frac{1}{0.4j} + \frac{1}{j0.1} \end{bmatrix}$$

By considering Y_{BUS1} as reference bus eliminate Row 1 & Column 1.

$$Y_{BUS} = \begin{bmatrix} 2 & \frac{1}{j0.5} + \frac{1}{j0.1} & \frac{-1}{j0.1} \\ 3 & -\frac{1}{j0.1} & \frac{1}{j0.4} + \frac{1}{j0.1} \end{bmatrix}$$

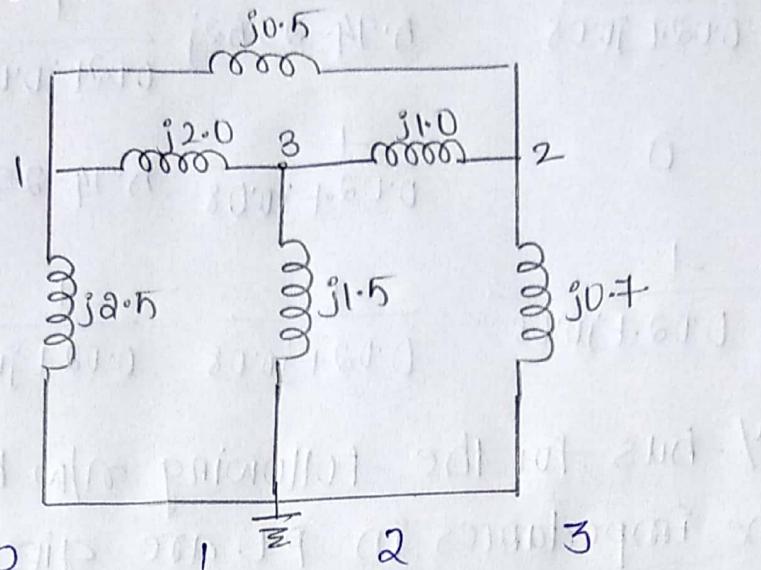
* Determine γ_{bus} by direct inspection method for the (5) following method as shown in below diagram. Given values are in per unit admittance.



$$\gamma_{\text{bus}} = \begin{bmatrix} 0 & j4.7 & -j2.5 & -j0.7 & -j1.5 \\ 1 & -j2.5 & j5 & -j0.5 & +j2.0 \\ 2 & -j0.7 & -j0.5 & j2.2 & -j1.0 \\ 3 & -j1.5 & -j2.0 & -j1.0 & j4.5 \end{bmatrix}$$


$$\gamma_{\text{bus}} = \begin{bmatrix} 1 & 2 & 3 \\ j5 & -j0.5 & -j2.0 \\ -j0.5 & j2.2 & -j1.0 \\ -j2.0 & -j1.0 & j4.5 \end{bmatrix}$$

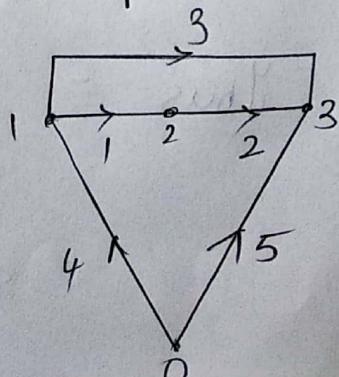* Consider the graph shown below which represents a four bus system each line has a series impedance of $0.02 + j0.08$ and line charging admittance of $j0.02$. Compute γ -bus by direct inspection method.



$$Y_{\text{Bus}} = \begin{bmatrix} 0 & 5.94 - j23.52j & \frac{-1}{0.02+j0.08} & 2 \\ 1 & \frac{-1}{0.02+j0.08} & 5.94 - j23.52j & \frac{-1}{0.02+j0.08} \\ 2 & 0 & \frac{-1}{0.02+j0.08} & 5.94 - j23.52j \\ 3 & \frac{-1}{0.02+j0.08} & \frac{-1}{0.02+j0.08} & \frac{-1}{0.02+j0.08} + 5.94j23.52 \end{bmatrix}$$

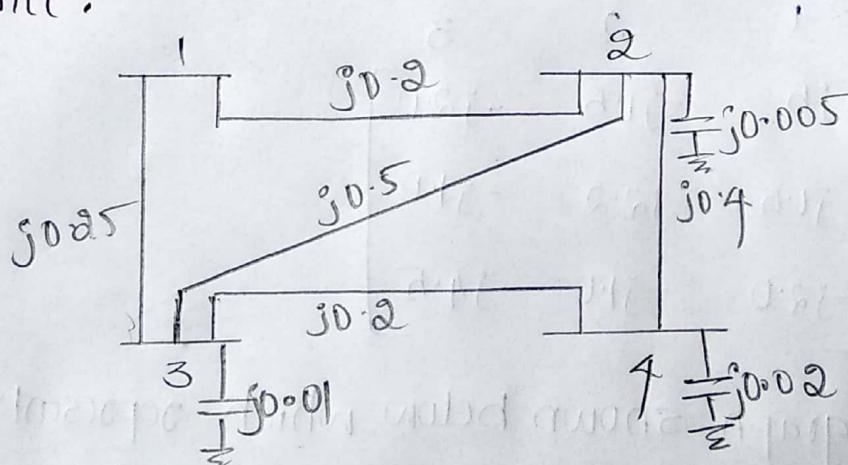* Compute Y-bus for the following n/w by direct inspection method. Line impedances in P.U are given in the n/w. Consider half line charging admittance at bus 2 is $j0.005$ and at bus 5 is $j0.01$ shunt capacitor admittance at bus 4 is $j0.02$. Compute Y-bus by singular transformation without considering half line charging admittance and shunt capacitor admittance.



$$Y_{\text{bus.}} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} & Y_{14} \\ Y_{21} & Y_{22} & Y_{23} & Y_{24} \\ Y_{31} & Y_{32} & Y_{33} & Y_{34} \\ Y_{41} & Y_{42} & Y_{43} & Y_{44} \end{bmatrix}$$

$$y_{11} = j0.2 + j0.25 = y_{12} + y_{13} = \frac{1}{j0.2} + \frac{1}{j0.25} = -j5 - j4 = -j9 \quad (6)$$

$$y_{12} = -\left(\frac{1}{j0.2}\right) = j5$$


$$y_{13} = -\left(\frac{1}{0.25}\right) = j4$$

$$y_{14} = 0.$$

$$Y_{bus} = \begin{bmatrix} -j9 & j5 & j4 & 0 \\ j5 & -j9.495 & j2 & j2.5 \\ j4 & j2 & -j16.99 & j5 \\ 0 & j2.5 & j5 & -j7.48 \end{bmatrix}$$


$$y_{33} = \frac{1}{j0.25} + \frac{1}{j0.5} + \frac{1}{j0.2} + j0.01 = -j10.99$$
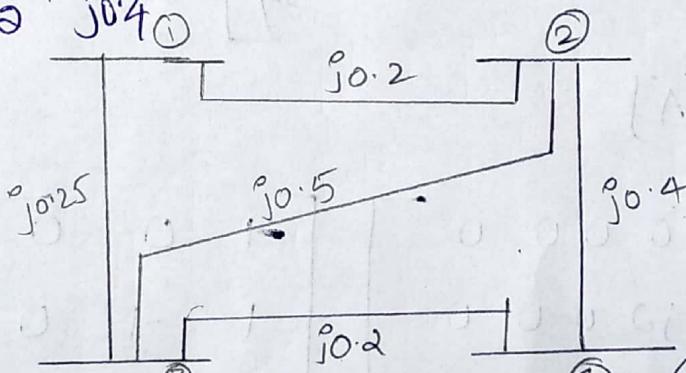
$$y_{44} = \frac{1}{j0.2} + \frac{1}{j0.4} + j0.02 = -j7.48$$



singular transformation

$$Y_{Bus} = A^t [Y] A$$

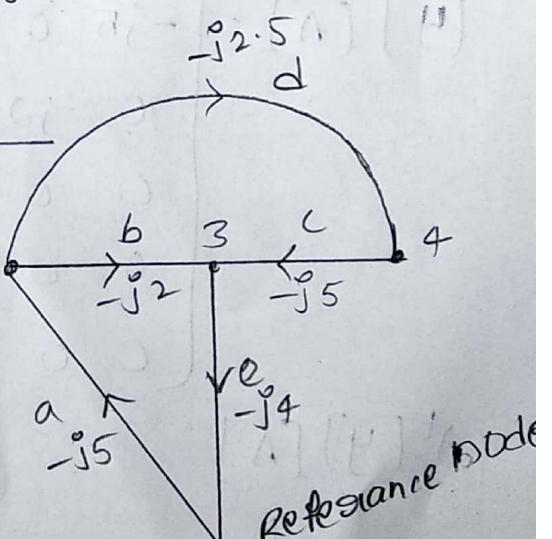

$$A = \begin{bmatrix} 2 & 3 & 4 & 0 \\ a & -1 & 0 & 0 \\ b & 1 & -1 & 0 \\ c & 0 & -1 & 1 \\ d & 1 & 0 & -1 \\ e & 0 & +1 & 0 \end{bmatrix} \Rightarrow A^t = \begin{bmatrix} 2 & a & b & c & d & e \\ 3 & -1 & 1 & 0 & 1 & 0 \\ 4 & 0 & -1 & -1 & 0 & 1 \\ 1 & 0 & 0 & 1 & -1 & 0 \end{bmatrix}$$

$$Y = b \begin{bmatrix} a & b & c & d & e \\ y_{aa} & 0 & 0 & 0 & 0 \\ 0 & y_{bb} & 0 & 0 & 0 \\ 0 & 0 & y_{cc} & 0 & 0 \\ 0 & 0 & 0 & y_{dd} & 0 \\ 0 & 0 & 0 & 0 & y_{ee} \end{bmatrix}$$

$$Y = \begin{bmatrix} -j5 & 0 & 0 & 0 & 0 \\ 0 & -j2 & 0 & 0 & 0 \\ 0 & 0 & -j5 & 0 & 0 \\ 0 & 0 & 0 & -j2.5 & 0 \\ 0 & 0 & 0 & 0 & -j4 \end{bmatrix}$$

$$Y_{\text{Bus}} = A^t [Y] [A]$$


$$[Y] [A] = \begin{bmatrix} -j5 & 0 & 0 & 0 & 0 \\ 0 & -j2 & 0 & 0 & 0 \\ 0 & 0 & -j5 & 0 & 0 \\ 0 & 0 & 0 & -j2.5 & 0 \\ 0 & 0 & 0 & 0 & -j4 \end{bmatrix} \begin{bmatrix} -1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & -1 & 1 \\ 1 & 0 & -1 \\ 0 & 1 & 1 \end{bmatrix}$$

$$A^t [Y] [A]$$

$$= \begin{bmatrix} j5 & 0 & 0 \\ -j2 & j2 & 0 \\ 0 & j5 & -j5 \\ -j2.5 & 0 & ja.5 \\ 0 & -j4 & -j4 \end{bmatrix} \begin{bmatrix} -1 & 1 & 0 & 1 & 0 \\ 0 & -1 & -1 & 0 & 1 \\ 0 & 0 & 1 & -1 & 0 \end{bmatrix}$$

$$Y_{bus} = \begin{bmatrix} -j5 & j5 & 0 & j5 & 0 \\ j2 & -j4 & -j2 & -j2 & j2 \\ 0 & -j5 & -j10 & j5 & j5 \\ ja.5 & -ja.5 & ja.5 & -ja.5 & 0 \\ 0 & j4 & 0 & j4 & -j4 \end{bmatrix}$$

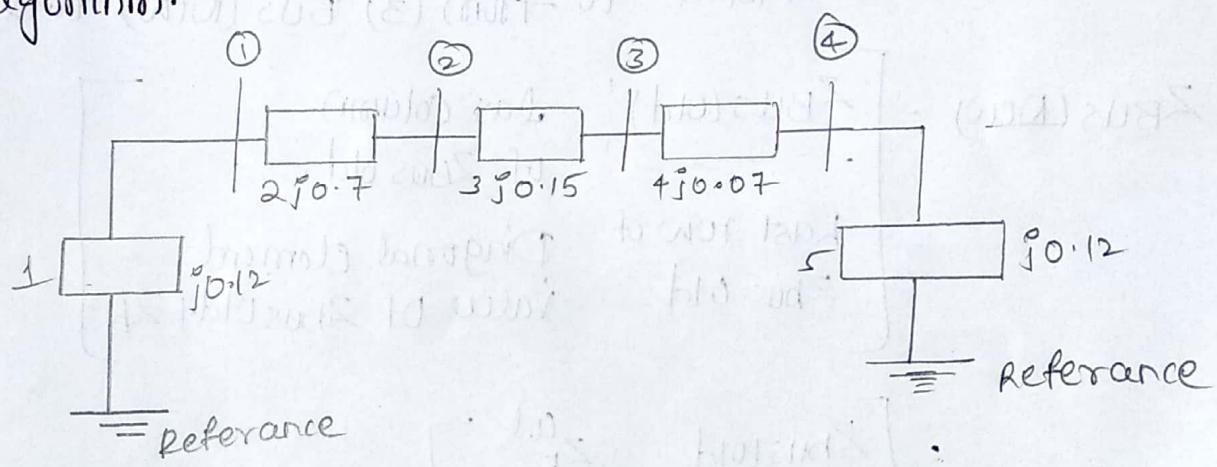
* Find bus incidence matrix for the following interconnected PS line impedances are in P.U by applying complete Z_{bus} algorithm.



Step 1: Element '1' is connected from Bus ① (New Bus) to

$$Z_{bus}(\text{new}) = \begin{bmatrix} 0 & 1 \\ 1 & \begin{bmatrix} 2j0.7 & 0 \\ 0 & 0 \end{bmatrix} \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 0 & j0.12 \end{bmatrix} \quad \text{reference}$$

Step 2:

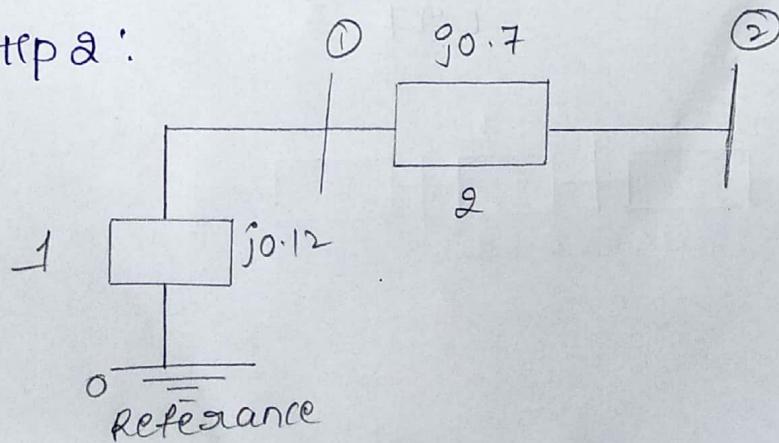


Element '2' is added from bus(2) to bus(1)

$$Z_{\text{BUS}}(\text{NEW}) = \begin{bmatrix} j0.12 & j0.12 \\ j0.12 & j0.12 + j0.7 \end{bmatrix}$$

$$Z_{\text{BUS}}(\text{NEW}) = j \begin{bmatrix} 0.12 & 0.12 \\ 0.12 & 0.82 \end{bmatrix}$$

Step 3:

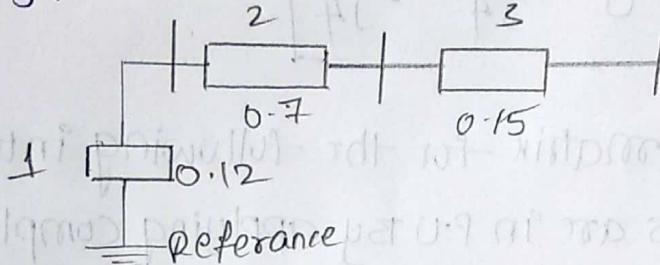


Element '3' is added to from (3) BUS (New) to (2)

$$Z_{\text{BUS}}(\text{NEW}) = \begin{bmatrix} Z_{\text{BUS}}(\text{old}) & \text{Last column of } Z_{\text{bus old}} \\ \dots & \text{Diagonal element value of } Z_{\text{bus old}} + Z_b \end{bmatrix}$$

$$= \begin{bmatrix} Z_{\text{bus old}} & Z_k^{\text{col}} \\ Z_k^{\text{row}} & Z_b + Z_k \end{bmatrix}$$


$$= j \begin{bmatrix} 1 & 2 & 3 \\ 0.12 & 0.12 & 0.12 \\ 0.12 & 0.82 & 0.82 \\ 0.12 & 0.82 & 0.82 + 0.15 \end{bmatrix}$$

Step 4 :

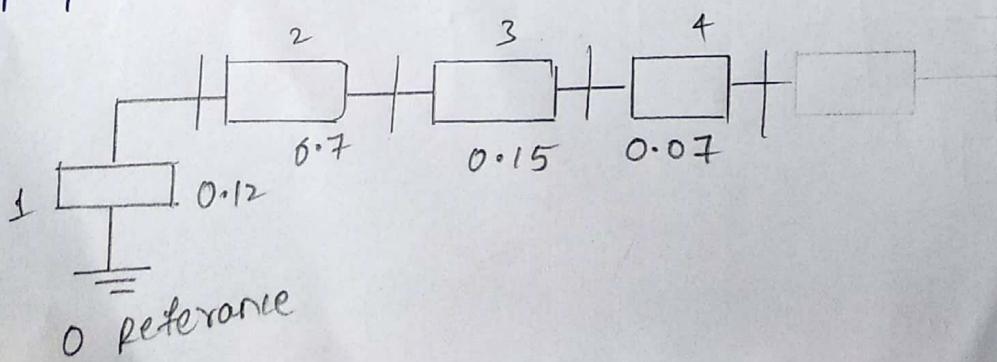

$$= j \begin{bmatrix} 0.12 & 0.12 & 0.12 & 0.12 \\ 0.12 & 0.82 & 0.82 & 0.82 \\ 0.12 & 0.82 & 0.97 & 0.97 \\ 0.12 & 0.82 & 0.97 & 0.97 + 0.07 \end{bmatrix}$$


Step 5:

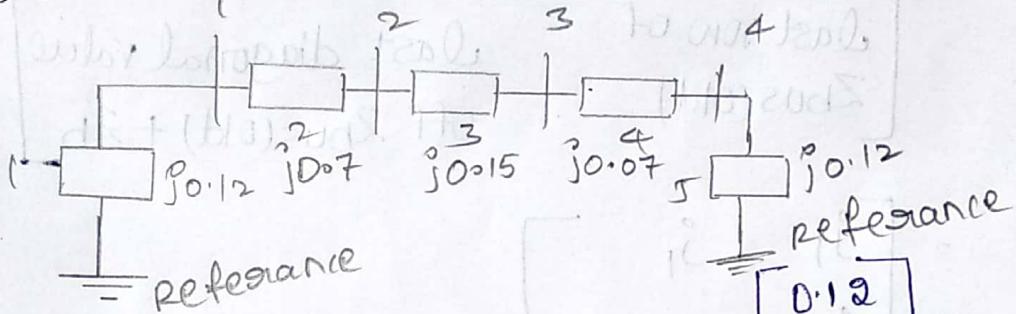

$$Z_{\text{BUS}}(\text{new}) = Z_{\text{BUS}}(\text{old}) - \frac{1.07 + j1}{1.04 + 0.12} \begin{bmatrix} 0.12 \\ 0.82 \\ 0.97 \end{bmatrix} \begin{bmatrix} 0.12 & 0.82 & 0.97 \end{bmatrix}$$

* Compute Z_{bus} by a) Z_{bus} algorithm method
b) Inversion of Y_{bus}

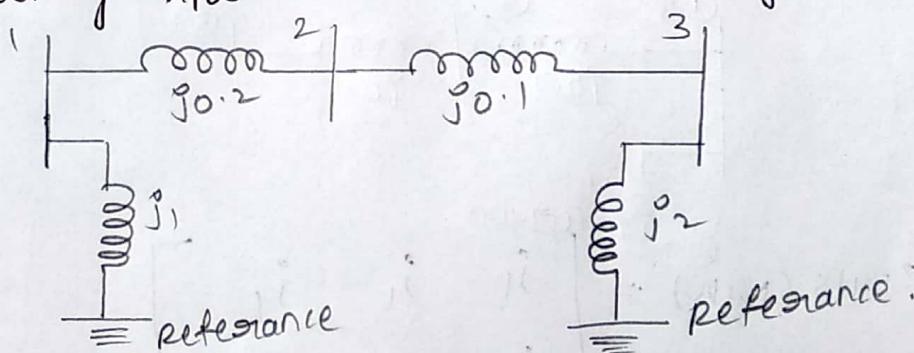For the following line reactances are given in per unit




Step 1: j_1 is added from bus(1) to ref bus(1)
is new bus

$$\begin{aligned} Z_{\text{BUS}}(\text{new}) &= \begin{bmatrix} 0 & Z_{\text{bus}}(\text{old}) & 0 \\ 0 & 0 & 0 \end{bmatrix} \\ &= \begin{bmatrix} 0 & 0 & 1 \\ 0 & 0 & j_1 \end{bmatrix} \end{aligned}$$

$$Z_{\text{BUS}}(\text{new}) = [j_1]$$

Step 2 :

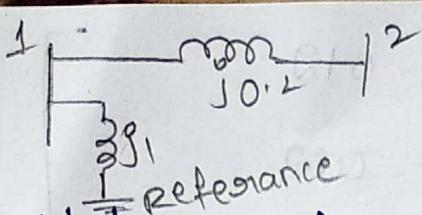


$j_{0.2}$ is added from bus 2 (new) to bus 1 (old)

$$Z_{\text{BUS}(\text{new})} = \begin{bmatrix} Z_{\text{bus}(\text{old})} & \text{last column of } Z_{\text{bus}(\text{old})} \\ \text{last row of } Z_{\text{bus}(\text{old})} & \begin{array}{l} \text{last diagonal value} \\ \text{off } Z_{\text{bus}(\text{old})} + Z_b \end{array} \end{bmatrix}$$

$$= \begin{bmatrix} j_1 & j_1 \\ j_1 & j_1 + j_{0.2} \end{bmatrix}$$


$$= \begin{bmatrix} j_1 & j_1 \\ j_1 & j_{1.2} \end{bmatrix}$$

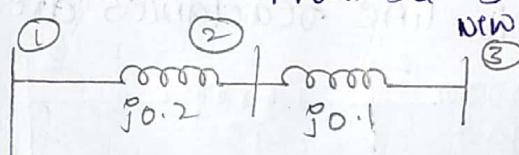Step 3 : $j_{0.1}$ is added from bus 3 to bus 2 (old)



$$Z_{\text{BUS}(\text{NEW})} = \begin{bmatrix} j_1 & j_1 & j_1 \\ j_1 & j_{1.2} & j_{1.2} \\ j_1 & j_{1.2} & j_{1.3} \end{bmatrix}$$

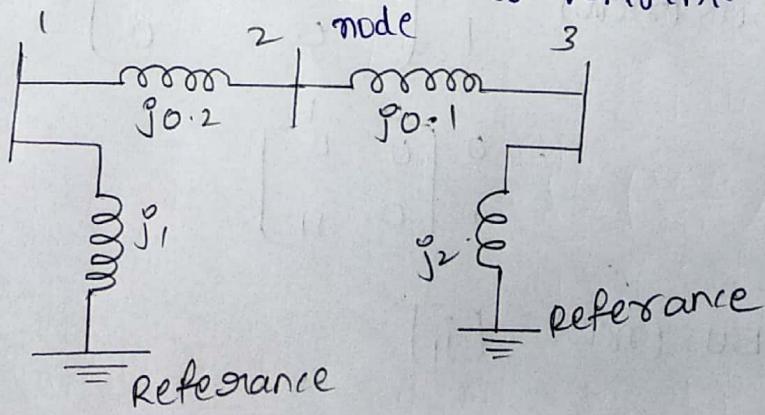Step 4 : j_2 is added from bus 3 to reference Bus 3 is old bus



$$Z_{bus}(\text{new}) = Z_{bus}(\text{old}) - \frac{\text{last diagonal value}}{\text{last diagonal value}} \begin{bmatrix} \text{last column of } Z_{bus} \text{ old} \end{bmatrix} \begin{bmatrix} \text{last row of } Z_{bus} \text{ old} \end{bmatrix}$$


$$\begin{bmatrix} j_1 & j_1 & j_1 \\ j_1 & j_{1,2} & j_{1,2} \\ j_1 & j_{1,2} & j_{1,3} \end{bmatrix} - \frac{1}{j_{1,3} + j_2} \begin{bmatrix} j_1 \\ j_{1,2} \\ j_{1,3} \end{bmatrix} \begin{bmatrix} j_1 & j_{1,2} & j_{1,3} \end{bmatrix}$$

$$= \begin{bmatrix} j_1 & j_1 & j_1 \\ j_1 & j_{1,2} & j_{1,2} \\ j_1 & j_{1,2} & j_{1,3} \end{bmatrix} - \frac{1}{j_{1,3} + j_2} \begin{bmatrix} -1 & -1 & -1 \\ -1 & -1 & -1 \\ -1 & -1 & -1 \end{bmatrix}$$

$$\begin{bmatrix} j_1 & j_1 & j_1 \\ j_1 & j_{1,2} & j_{1,2} \\ j_1 & j_{1,2} & j_{1,3} \end{bmatrix} - \frac{1}{j_{1,3} + j_2} \begin{bmatrix} -0.3 & -0.36 & -0.39 \\ -0.36 & -0.43 & -0.47 \\ -0.39 & -0.47 & -0.51 \end{bmatrix}$$

$$(H)_{11} = j \begin{bmatrix} 1 & 1 & 1 \\ 1 & 1 & 1 \\ 1 & 1 & 1 \end{bmatrix} - j \begin{bmatrix} 0.3 & 0.36 & 0.39 \\ 0.36 & 0.43 & 0.47 \\ 0.39 & 0.47 & 0.51 \end{bmatrix}$$

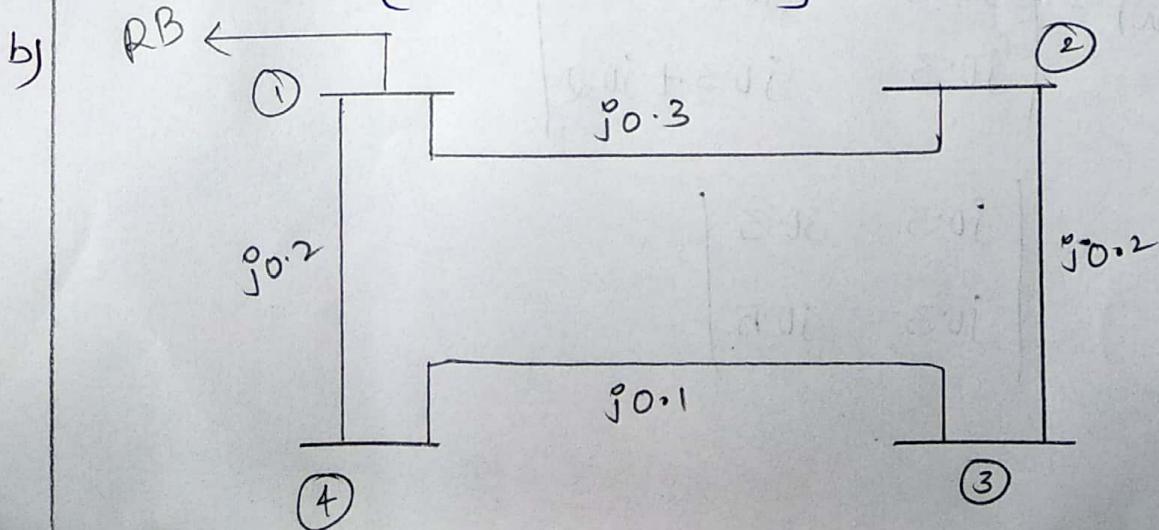
$$= j \begin{bmatrix} 0.7 & 0.64 & 0.61 \\ 0.64 & 0.57 & 0.53 \\ 0.61 & 0.53 & 0.49 \end{bmatrix}$$



Step 1: Add $j0.3$ from Bus ③ to Reference bus(1)

Let us consider bus(1) as reference bus

Reference bus

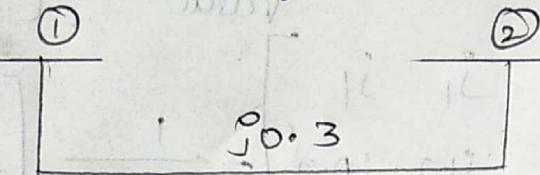

$$Z_{\text{bus}(\text{new})} = \begin{vmatrix} 1 & 2 \\ Z_{\text{bus}(\text{old})} & 0 \\ 2 & 0 + Z_b \end{vmatrix} = \begin{vmatrix} 1 & 0 & 0 \\ 0 & 1 & j0.3 \\ 0 & j0.3 & 1 \end{vmatrix}$$

Step 2: Add $j0.2$ from Bus old(2) to bus New(3)

$$Z_{\text{bus}(\text{new})} = \begin{vmatrix} Z_{\text{bus}(\text{old})} & Z_k^{\text{column}} \\ Z_k^{\text{row}} & Z_{kk} + Z_b \end{vmatrix}$$

where

Z_k^{row} = Last row of Z_{old} (except last diagonal of Z_{old})

Z_k^{col} = Last col of Z_{old} (except last diagonal of Z_{old})

Z_{kk} = Last diagonal of Z_{old}

Z_b = element Impedance

$$Z_{\text{bus}(\text{new})} = \begin{vmatrix} j0.3 & j0.3 \\ j0.3 & j0.3 + j0.2 \end{vmatrix}$$

$$= \begin{vmatrix} j0.3 & j0.3 \\ j0.3 & j0.5 \end{vmatrix}$$

Step 3: Add $j0.1$ from Bus(3) Old to reference bus(4) New (10)

$$Z_{\text{BUS}(\text{New})} = \begin{vmatrix} Z_{\text{BUS}(\text{old})} & Z_k^{\text{col}} \\ Z_k^{\text{row}} & Z_{kk} + Z_b \end{vmatrix}$$
$$= \begin{vmatrix} j0.3 & j0.3 & j0.3 \\ j0.3 & j0.5 & j0.5 \\ j0.3 & j0.5 & j0.6 \end{vmatrix}$$

Step 4:

$$Z_{\text{BUS}(\text{New})} = Z_{\text{BUS}(\text{old})} \cdot \frac{1}{Z_{kk} + Z_b} \begin{bmatrix} Z_k^{\text{col}} \\ Z_k^{\text{row}} \end{bmatrix}$$
$$= \begin{bmatrix} j0.3 & j0.3 & j0.3 \\ j0.3 & j0.5 & j0.5 \\ j0.5 & j0.5 & j0.6 \end{bmatrix} \cdot \frac{1}{j0.5} \begin{bmatrix} j0.3 \\ j0.5 \end{bmatrix} \begin{bmatrix} j0.3 & j0.5 \end{bmatrix}$$