

# Resonant Grounding

NEUTRAL GROUNDING, POWER SYSTEM


0

## Resonant Grounding or Arc Suppression Coil Grounding:

We have seen that capacitive currents are responsible for producing arcing grounds. These capacitive currents flow because capacitance exists between each line and earth. If inductance  $L$  of appropriate value is connected in parallel with the capacitance of the system, the fault current  $I_F$  flowing through  $L$  will be in phase opposition to the capacitive current  $I_C$  of the system. If  $L$  is so adjusted that  $I_L = I_C$  then resultant current in the fault will be zero. This condition is known as Resonant Grounding.

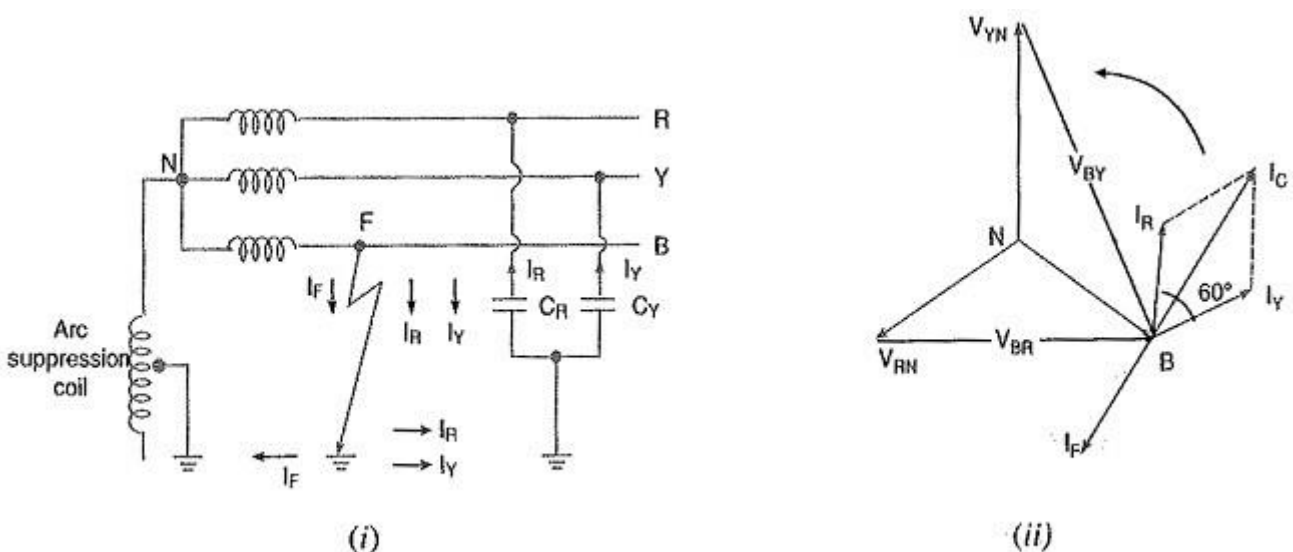**When the value of  $L$  of arc suppression coil is such that the fault current  $I_F$  exactly balances the capacitive current  $I_C$ , it is called Resonant Grounding.**

**Circuit details:** An arc suppression coil (also called **Peterson coil**) is an iron-cored coil connected between the neutral and earth as shown in Fig. 26.160). The reactor is provided with tapping to change the inductance of the coil. By adjusting the tapplings on the coil, the coil can be tuned with the capacitance of the system i.e. resonant grounding can be achieved.



**Operation:** Fig. 26.160) shows the 3-phase system employing Peterson coil grounding. Suppose line to ground fault occurs in the line B at point F. The fault current  $I_F$  and capacitive currents  $I_R$  and  $I_Y$  will flow as shown in Fig. 26.160). Note that  $I_F$  flows through the Peterson coil (or Arc suppression coil) to neutral and back through the fault. The total capacitive current  $I_C$  is the phasor sum of  $I_R$  and  $I_Y$  as shown in phasor diagram in Fig. 26.16(ii). The voltage of the faulty phase is applied across the arc suppression coil. Therefore, fault current  $I_F$  lags the faulty phase voltage by  $90^\circ$ . The current  $I_F$  is in phase opposition to capacitive current  $I_C$  [See Fig. 26.16(ii)]. By adjusting the tapplings on the

Peterson coil, the resultant current in the fault can be reduced, If inductance of the coil is so adjusted that  $I_L = I_C$  then resultant current in the fault will be zero.

**Value of L for [resonant grounding](#):** For [resonant grounding](#), the system behaves as an ungrounded neutral system. Therefore, full line voltage appears across capacitors  $C_R$  and  $C_Y$ .

$$I_R = I_Y = \frac{\sqrt{3}V_{ph}}{X_C}$$

$$I_C = \sqrt{3} I_R = \sqrt{3} \times \frac{\sqrt{3}V_{ph}}{X_C} = \frac{3V_{ph}}{X_C}$$

Here,  $X_C$  is the line to ground capacitive reactance.

$$I_F = \frac{V_{ph}}{X_L}$$

Here,  $X_L$  is the inductive reactance of the arc suppression coil.

For [resonant grounding](#),

$$I_L = I_C$$

$$\frac{V_{ph}}{X_L} = \frac{3V_{ph}}{X_C}$$

$$X_L = \frac{X_C}{3}$$

$$\omega L = \frac{1}{3\omega C}$$

$$L = \frac{1}{3\omega^2 C} \quad \dots(i)$$

Exp. (i) gives the value of inductance L of the arc suppression coil for [resonant grounding](#).

### The Peterson coil grounding has the following advantages:

- ♦ The Peterson coil is completely effective in preventing any damage by an arcing ground. The Peterson coil has the advantages of [ungrounded neutral system](#).

### The Peterson coil grounding has the following disadvantages :

- ♦ Due to varying operational conditions, the capacitance of the network changes from time to time. Therefore, inductance L of Peterson [coil](#) requires readjustment.
- ♦ The lines should be transposed.

## MORE RELATED ARTICLE

[System Grounding](#)

[Grounding or Earthing](#)